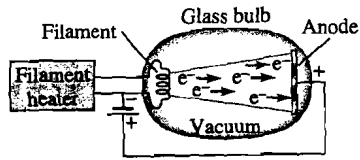


3. (a) What is the direction of the current in the vacuum tube shown in the figure? (b) Electrons hit the anode at a rate of  $6.0 \times 10^{12}$  per second. What is the current in the tube?



- a) current flows opposite electron movement  
 $\therefore$   $\leftarrow I$  anode to filament

$$b) \quad 6.0 \times 10^{12} \frac{\text{electrons}}{\text{sec}}$$

$$I = \frac{\text{charge}}{\text{time}}$$

$$= \frac{(1.6 \times 10^{-19} \text{ C}) \times 6.0 \times 10^{12} \frac{\text{e}}{\text{s}}}{1 \text{ s}}$$

$$= 9.6 \times 10^{-7} \frac{\text{C}}{\text{s}}$$

$$I = 9.6 \times 10^{-7} \text{ A} \quad \text{or} \quad 0.96 \mu\text{A}$$

10. The label on a 12.0-V truck battery states that it is rated at 180.0 A·h (ampere-hours). Treat the battery as ideal.  
 (a) How much charge in coulombs can be pumped by the battery? [Hint: Convert A·h to A·s.] (b) How much electric energy can the battery supply? (c) Suppose the radio in the truck is left on when the engine is not running. The radio draws a current of 3.30 A. How long does it take to drain the battery if it starts out fully charged?

$$a) \quad Q = ?$$

$$180 \text{ A} \cdot \text{h} \times \frac{3600 \text{ s}}{\text{h}}$$

$$= 648000 \text{ A} \cdot \text{s}$$

$$= 648000 \frac{\text{C}}{\text{s}} \cdot \text{s}$$

$$Q = 6.48 \times 10^5 \text{ C}$$

$$b) \quad \text{Energy} = qV$$

$$= (6.48 \times 10^5 \text{ C})(12.0 \text{ V})$$

$$= 7.78 \times 10^6 \text{ J}$$

$$E = 7.78 \text{ MJ}$$

$$c) \quad I = 3.30 \text{ Amp} = 3.30 \frac{\text{C}}{\text{s}}$$


$$I = \frac{\text{charge}}{\text{time}} = \frac{Q}{t}$$

$$t = \frac{Q}{I} = \frac{6.48 \times 10^5 \text{ C}}{3.30 \text{ C/s}}$$

$$= 1.96 \times 10^5 \text{ s} \times \frac{1 \text{ h}}{3600 \text{ s}}$$

$$\text{time} = 54.5 \text{ hours}$$

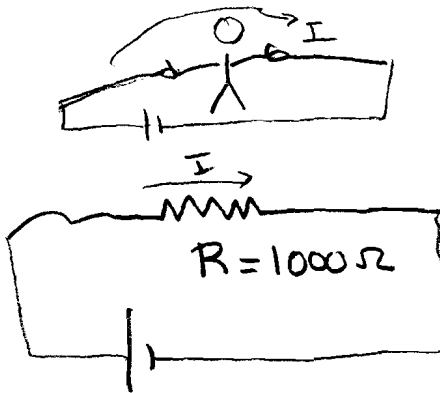25. A person can be killed if a current as small as 50 mA passes near the heart. An electrician is working on a humid day with hands damp from perspiration. Suppose his resistance from one hand to the other is  $1 \text{ k}\Omega$  and he is touching two wires, one with each hand. (a) What potential difference between the two wires would cause a 50-mA current from one hand to the other? (b) An electrician working on a "live" circuit keeps one hand behind his or her back. Why?




$$\begin{aligned} \text{a)} \quad V &= IR \\ &= (50 \times 10^{-3} \text{ A})(1 \times 10^3 \Omega) \\ &= 50 \text{ V} \end{aligned}$$

- b) With one hand in a pocket the electrician can't create a circuit between their hands which would allow current to flow across the heart



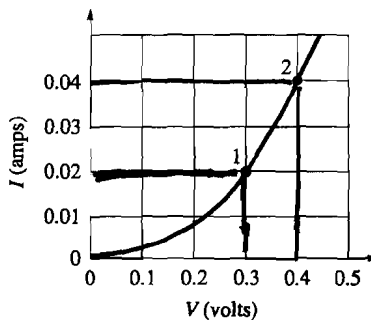26. An electric device has the current-voltage ( $I$ - $V$ ) graph shown. What is its resistance at (a) point 1 and (b) point 2? [Hint: Use the definition of resistance.]



$$\text{a)} \quad V = IR$$

$$R = \frac{V}{I}$$

at point ①

$$I = 0.02 \text{ A} \quad V = 0.3 \text{ V}$$


$$R = \frac{0.3 \text{ V}}{0.02 \text{ A}} = 15 \Omega$$

b) point ②

$$I = 0.04 \text{ A} \quad V = 0.4 \text{ V}$$

$$R = \frac{V}{I} = \frac{0.4 \text{ V}}{0.04 \text{ A}} = 10 \Omega$$

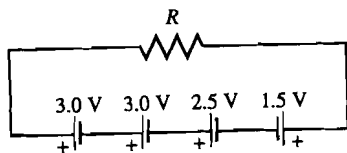37. Suppose four batteries are connected in series as shown.  
 (a) What is the equivalent emf of the set of four batteries? Treat them as ideal sources of emf. (b) If the current in the circuit is 0.40 A, what is the value of the resistor  $R$ ?



a) Voltages in series add

$$\begin{aligned} \mathcal{E}_{\text{eq}} &= \sum \mathcal{E}_i \\ &= \mathcal{E}_1 + \mathcal{E}_2 + \mathcal{E}_3 + \mathcal{E}_4 \\ &= 3.0\text{V} + 3.0\text{V} + 2.5\text{V} + 1.5\text{V} \end{aligned}$$


$$\mathcal{E}_{\text{eq}} = 7.0\text{V}$$

note  $\mathcal{E}_4$  is opposite the other 3 batteries

b)  $V = IR$

$$R = \frac{V}{I} = \frac{7\text{V}}{0.4\text{A}} = 17.5 \Omega \approx 18 \Omega = R$$

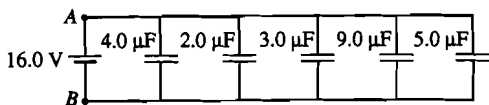39. (a) Find the equivalent capacitance between points A and B for the five capacitors. (b) If a 16.0-V emf is connected to the terminals A and B, what is the charge on a single equivalent capacitor that replaces all five? (c) What is the charge on the 3.0- $\mu\text{F}$  capacitor?



a) Capacitors in parallel add

$$C_{\text{eq}} = C_1 + C_2 + C_3 + \dots$$

$$\begin{aligned} C_{\text{eq}} &= 4.0\mu\text{F} + 2.0\mu\text{F} + 3.0\mu\text{F} \\ &\quad + 9.0\mu\text{F} + 5.0\mu\text{F} \end{aligned}$$

$$C_{\text{eq}} = 23\mu\text{F}$$

b)  $Q = C \Delta V = C_{\text{eq}} \Delta V$   
 $= (23 \times 10^{-6} \text{F})(16.0\text{V})$

$$Q = 368 \mu\text{C}$$


c)  $Q = C \Delta V = (3 \times 10^{-6} \text{F})(16.0\text{V})$

$$Q = 48 \mu\text{C}$$

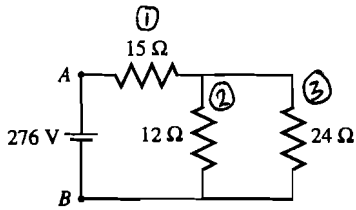40. (a) What is the equivalent resistance between points A and B? (b) A 276-V emf is connected to the terminals A and B. What is the current in the 12-Ω resistor?

$$R_{eq \text{ series}} = R_1 + R_2$$

$$\frac{1}{R_{eq \text{ parallel}}} = \frac{1}{R_1} + \frac{1}{R_2}$$



a) Resistors ② and ③ are in parallel (12Ω and 24Ω)

$$\frac{1}{R_{eq1}} = \frac{1}{R_1} + \frac{1}{R_2}$$

find a common denominator


$$\frac{1}{R_{eq1}} = \frac{R_2 + R_1}{R_1 R_2}$$

now we can invert both sides of the equation

$$R_{eq1} = \frac{R_1 R_2}{R_1 + R_2} = \frac{(12\Omega)(24\Omega)}{12\Omega + 24\Omega} = \frac{288\Omega^2}{36\Omega} = 8\Omega$$

Notice that the equivalent resistance is less than either resistor!


Now we have

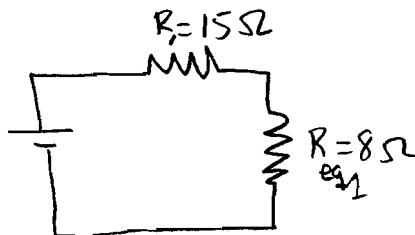


These are in series so

$$R_{eq2} = R_1 + R_{eq1} = 15\Omega + 8\Omega = 23\Omega = R_{eq2}$$

So

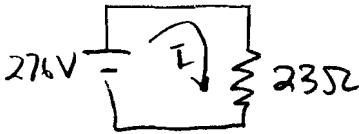

↓ series

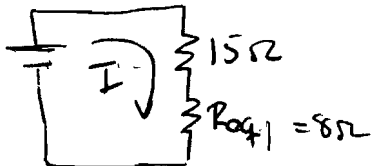


$$V = IR_{eq2} \quad I = \frac{V}{R} = \frac{276V}{23\Omega} = 12A$$

The current through both resistors  $R_1$  and  $R_{eq1}$  is the same as  $R_{eq2}$ . Since it is formed from the series combination.

The voltage across  $R_{eq2}$

$$V = IR_{eq1} = (12A)(8\Omega) = 96V$$

40 continues


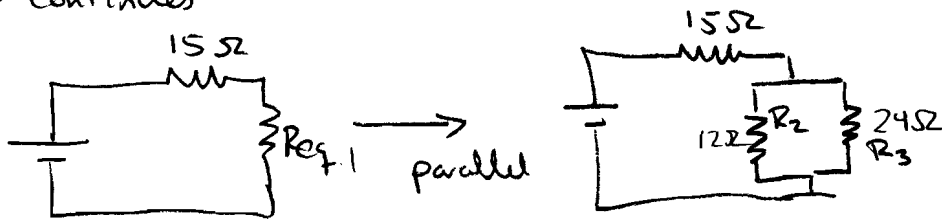


The voltage across  $R_2 =$  Voltage across  $R_3$  since they are in parallel -


It is also equal to the voltage across  $R_{eq1}$  since they are formed from the parallel combination

$$I = \frac{V}{R_2} = \frac{96V}{12\Omega} = \boxed{8.0A = I}$$

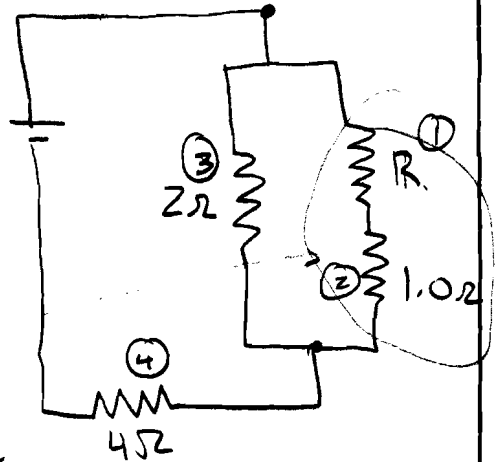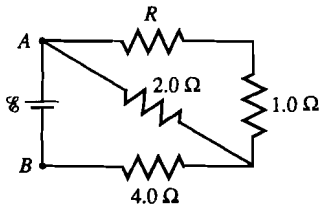41. (a) What is the equivalent resistance between points A and B if  $R = 1.0 \Omega$ ? (b) If a 20-V emf is connected to the terminals A and B, what is the current in the 2.0- $\Omega$  resistor?





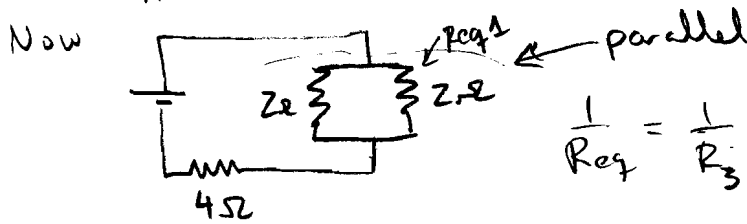a) series  $R_{eq1} = R + 1.0 \Omega = 1.0 \Omega + 1.0 \Omega = 2.0 \Omega$



$$\frac{1}{R_{eq2}} = \frac{1}{R_3} + \frac{1}{R_{eq1}} = \frac{1}{2 \Omega} + \frac{1}{2 \Omega} = \frac{1}{1 \Omega}$$


$R_{eq2} = 1 \Omega$

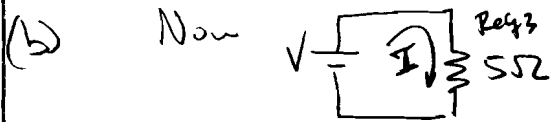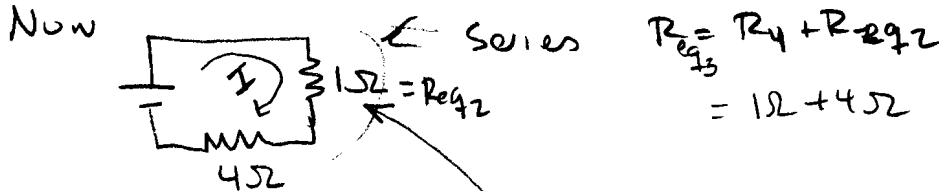

$$I = \frac{V}{R} = \frac{20V}{5 \Omega} = 4A = \text{current through } R_{eq3}$$

So the current through  $R_{eq2} = 1 \Omega$  is 4A since  $R_{eq2}$  is in series with  $R_4$



$$V = I R_{eq2} = (4A)(1 \Omega) = 4V$$

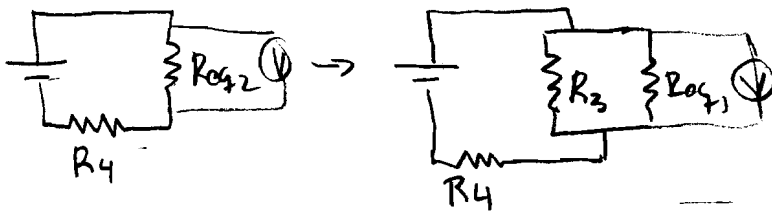

$$I = \frac{V}{R_3} = \frac{4V}{2 \Omega} = 2A = I$$


The voltage across  $R_{eq2}$  is the same as the voltage across  $R_3$  and  $R_{eq1}$  since they are a parallel combination

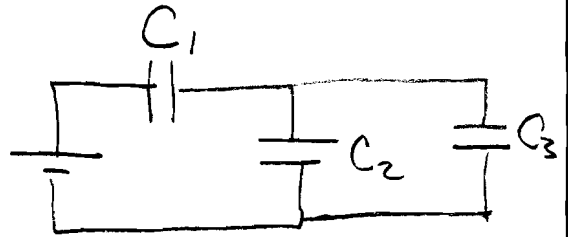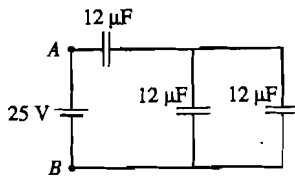49. (a) Find the value of a single capacitor to replace the three capacitors in the diagram. (b) What is the potential difference across the  $12\text{-}\mu\text{F}$  capacitor at the left side of the diagram? (c) What is the charge on the  $12\text{-}\mu\text{F}$  capacitor to the far right side of the circuit?



a)  $C_2$  and  $C_3$  are in parallel  $\therefore C_{eq1} = C_2 + C_3 = 12\mu\text{F} + 12\mu\text{F}$


$$C_{eq1} = 24\mu\text{F}$$

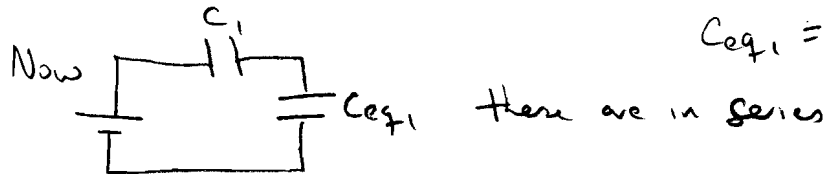

$$\frac{1}{C_{eq2}} = \frac{1}{C_1} + \frac{1}{C_{eq1}} \Rightarrow C_{eq2} = \frac{C_1 C_{eq1}}{C_1 + C_{eq1}} = \frac{(12\mu\text{F})(24\mu\text{F})}{36\mu\text{F}}$$


$$C_{eq2} = 8\mu\text{F}$$

b) Looking for  $\Delta V_1$

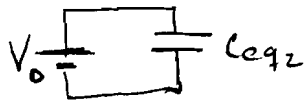

$$Q = C \Delta V_1 = (8\mu\text{F}) 25\text{V} = 200\mu\text{C}$$

charges are the same in series

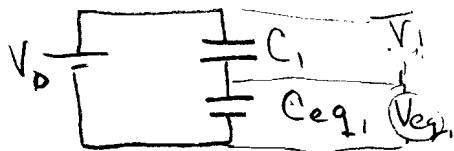

So  $Q$  on  $C_{eq1} = Q$  on  $C_{eq2}$

The voltage across  $C_1 = V_1$

$$V_1 = \frac{Q}{C_1} = \frac{200\mu\text{C}}{12\mu\text{F}} = 16.7\text{V}$$

The charge on the  $12\mu\text{F}$  capacitor on the far right or  $C_3$

The voltage across  $C_3$  is the same

as the voltage across  $C_{eq1}$  or  $V_0 - V_1 = 25\text{V} - 16.7\text{V} = 8.33\text{V}$ .

$$Q = C_3 \Delta V = (12\mu\text{F})(8.33\text{V})$$

$$Q_3 = 100\mu\text{C}$$

62. A portable CD player does not have a power rating listed, but it has a label stating that it draws a maximum current of 250.0 mA. The player uses three 1.50-V batteries connected in series. What is the maximum power consumed?

$$I = 250.0 \text{ mA}$$

Three 1.50 V batteries in series

$$V = V_1 + V_2 + V_3 = 3V = 3(1.50V) = 4.5V$$

$$P = IV = (250 \times 10^{-3} \text{ A})(4.5 \text{ V})$$


$$P = 1.125 \text{ W}$$




# Chapter 18

66. (a) What is the equivalent resistance if  $R_1 = 10.0 \Omega$  and  $R_2 = 15.0 \Omega$   
 (b) What current flows through  $R_1$   
 (c) What is the voltage drop across  $R_2$ ?  
 (d) What current flows through  $R_2$ ?  
 (e) How much power is dissipated in  $R_2$ ?


a)

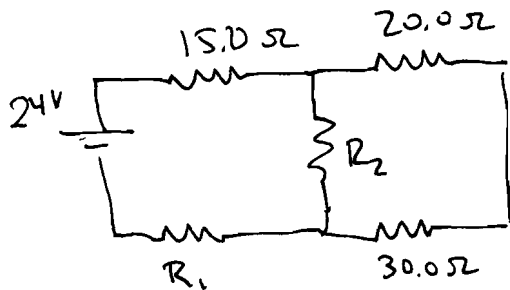

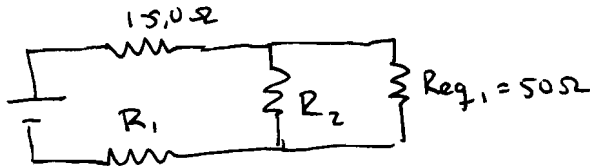The  $20 \Omega$  and  $30 \Omega$  are in series so  $R_{eq1} = 20 \Omega + 30 \Omega = 50 \Omega$



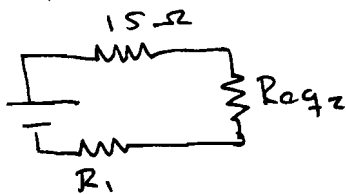$R_{eq1}$  and  $R_2$  are in parallel so  $R_{eq2} = \left( \frac{1}{R_{eq1}} + \frac{1}{R_2} \right)^{-1} = \left( \frac{1}{50} + \frac{1}{15} \right)^{-1} = 11.5 \Omega$



$R_1$ ,  $R_{eq2}$  and  $15 \Omega$  are in series so

$$R_{eq3} = R_1 + 15 \Omega + R_{eq2} = 10 \Omega + 15 \Omega + 11.5 \Omega =$$

$$R_{eq3} = 36.5 \Omega$$



- b) The current flowing through  $R_{eq3}$  = The current through  $R_1$  since  $R_{eq3}$  is formed from  $R_1$  in series.


$$I = \frac{V}{R} = \frac{24V}{36.5 \Omega} = 0.66 A = I_1$$

# Chapter 18


0.66  
c)



series

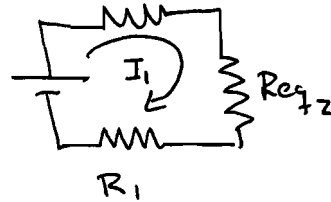

parallel

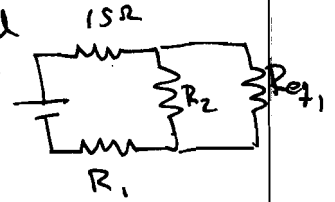

The voltage across  $R_{eq2}$  is  
The same as the voltage across  $R_2$  and  $R_{eq1}$

$$V_{R_{eq2}} = I_1 R_{eq2} = (0.66 \text{ A})(11.5 \Omega) = \boxed{7.55 \text{ V}} = V_2$$

d) The current through  $R_2$

$$V_2 = I_2 R_2 \quad I_2 = \frac{V_2}{R_2} = \frac{7.55 \text{ V}}{15 \Omega} = \boxed{0.5 \text{ A} = I_2}$$

Aside:

Why isn't the current

0.66 A ? Because it splits between  $R_2$  and  $R_{eq1}$   
because of the junction.

e) Power in  $R_2$   $P = I_2 V_2 = (0.5 \text{ A})(7.55 \text{ V})$

$$\boxed{P = 3.77 \text{ W}}$$