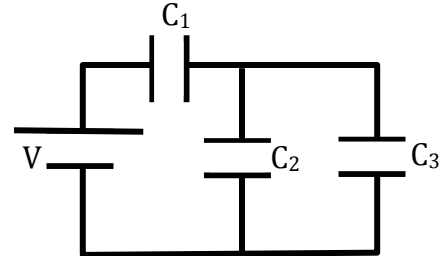


We can treat circuits with capacitors in similar way to the circuits with resistors. We still find that voltages across parallel elements are the same. Now instead of having currents in series elements be the same, charges are the same. We can use a similar methodology where we reduce the sets of capacitors to an equivalent capacitance and use the ideas of series charge being the same and parallel voltages being the same. We can use the following set of equations.

In this circuit, $C_1=2.0\mu\text{F}$, $C_2=1.0\mu\text{F}$, $C_3=3.0\mu\text{F}$, and $V=20\text{V}$.

$$Q = CV \quad \frac{1}{C_{\text{series}}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$


$$C_{||} = C_1 + C_2 + C_3$$



Begin by reducing C_2 and C_3 to an equivalent capacitance and redraw the circuit.

Resolve the parallel set: $C_{23} = C_2 + C_3$

$$C_{23} = 1.0 + 3.0 = 4.0 \mu\text{F}$$

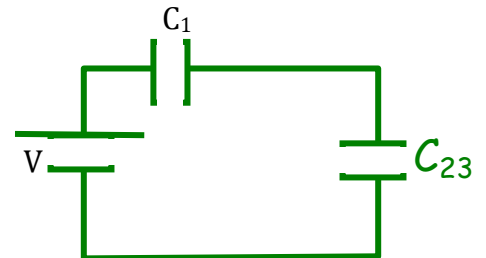


Next reduce the remaining capacitors to one and redraw the circuit.

Remaining capacitors are in series:

$$\frac{1}{C_{123}} = \frac{1}{C_1} + \frac{1}{C_{23}}$$
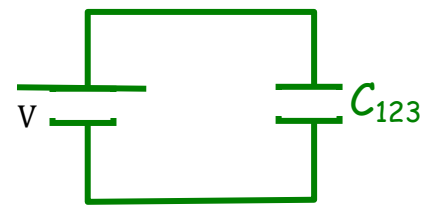
$$C_{123} = \frac{C_1 C_{23}}{C_1 + C_{23}} = \frac{(2)(4)}{(2) + (4)} = 1.33 \mu\text{F}$$



Now use the idea that series capacitors have the same charge and parallel capacitors have the same voltage to find the charge, Q , and the voltage, V , on each of the capacitors.

Charges on C_1 and C_{23} are equal and equal to that on C_{123} $Q_1 = Q_{23} = Q_{123}$

$$V - \frac{Q_1}{C_1} - \frac{Q_{23}}{C_{23}} = V - \frac{Q_{123}}{C_1} + \frac{Q_{123}}{C_{23}} = V - Q_{123} \left(\frac{1}{C_1} + \frac{1}{C_{23}} \right) = 0$$

$$Q_1 = Q_{23} = VC_{123} = (20\text{V})(1.33\mu\text{F}) = 26.6 \mu\text{C}$$

Voltages across C_1 and C_{23} are not equal and sum to V

$$V_1 = \frac{Q_{123}}{C_1} \quad \& \quad V_{23} = \frac{Q_{123}}{C_{23}}$$

$$\left. \begin{aligned} V_1 &= \frac{Q_{123}}{C_1} = \frac{26.6 \mu\text{C}}{2.0 \mu\text{F}} = 13.3 \text{ V} \\ V_{23} &= \frac{Q_{123}}{C_{23}} = \frac{26.6 \mu\text{C}}{4.0 \mu\text{F}} = 6.65 \text{ V} \end{aligned} \right\} V_1 + V_{23} = V$$

Voltages across C_2 and C_3 are equal and equal to that on C_{23}

$$V_{23} = V_2 = V_3 = 6.65 \text{ V}$$

Charges on C_1 and C_{23} are not equal and sum to Q_{23}

$$Q_{123} = \frac{V_{23}}{C_{23}} = Q_2 + Q_3$$

$$\left. \begin{aligned} Q_2 &= V_{23} C_2 = (6.65 \text{ V})(1 \mu\text{F}) = 6.65 \mu\text{C} \\ Q_3 &= V_{23} C_3 = (6.65 \text{ V})(3 \mu\text{F}) = 19.95 \mu\text{C} \end{aligned} \right\} Q_2 + Q_3 = Q_{23}$$

Summarize the capacitance, charge and voltage of each capacitor

