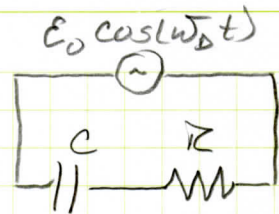


MT3 Pr 3-24

An electrical circuit has R & C in series with $\mathcal{E} = \mathcal{E}_0 \cos(\omega_D t)$, Find $I(t)$ and show it goes to zero as $\omega_D \rightarrow 0$



The D.E. is

$$R\dot{Q} + \frac{1}{C}Q = \mathcal{E}_0 \cos(\omega_D t)$$

GUESS

$$Q(t) = A \sin(\omega_D t) + B \cos(\omega_D t)$$

$$\dot{Q}(t) = A\omega_D \cos(\omega_D t) - B\omega_D \sin(\omega_D t)$$

STUFF THESE INTO THE DE

$$R\omega_D [A \cos(\omega_D t) - B \sin(\omega_D t)] + \frac{1}{C} [A \sin(\omega_D t) + B \cos(\omega_D t)] = \mathcal{E}_0 \cos(\omega_D t)$$

EQUATE COEFFICIENTS OF $\cos(\omega_D t)$ AND $\sin(\omega_D t)$

$$R\omega_D A + \frac{1}{C} B = \mathcal{E}_0$$

$$-R\omega_D B + \frac{1}{C} A = 0 \Rightarrow A = CR\omega_D B$$

$$R\omega_D (CR\omega_D B) + \frac{1}{C} B = \mathcal{E}_0$$

$$(C^2 R^2 \omega_D^2 + \frac{1}{C}) B = \mathcal{E}_0$$

$$\boxed{B = \frac{C \mathcal{E}_0}{C^2 R^2 \omega_D^2 + 1}} \Rightarrow \boxed{A = \frac{C^2 R \omega_D \mathcal{E}_0}{C^2 R^2 \omega_D^2 + 1}}$$

Thus

$$Q(t) = \frac{C \mathcal{E}_0}{C^2 R^2 \omega_D^2 + 1} [CR\omega_D \sin(\omega_D t) + \cos(\omega_D t)]$$

AND

$$\boxed{I(t) = \frac{C \mathcal{E}_0 \omega_D}{C^2 R^2 \omega_D^2 + 1} [CR\omega_D \cos(\omega_D t) - \sin(\omega_D t)]}$$

AND AS $\omega_D \rightarrow 0$, THE NUMERATOR IN THE FIRST FACTOR GOES TO ZERO AND $I(t) \rightarrow 0$