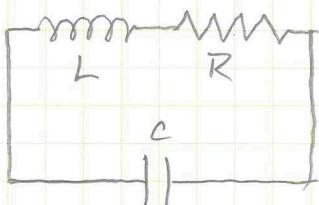


COMPUTE THE OSCILLATION FREQUENCIES, PERIODS, AND AMPLITUDE AFTER 2 PERIODS (AS A FRACTION OF A_0) FOR THE CIRCUIT SHOWN WITH $L = 0.01 \text{ H}$, $C = 10 \mu\text{F}$ AND $R = 10 \Omega$.



KIRCHHOFF'S RULE GIVES

$$\begin{aligned} L \ddot{Q} + R \dot{Q} + \frac{1}{C} Q &= 0 \\ \Rightarrow \ddot{Q} + 2\beta \dot{Q} + \omega_N^2 Q &= 0 \quad \beta = \frac{R}{2L}, \quad \omega_N^2 = \frac{1}{LC} \\ \Rightarrow Q(t) &= A_0 e^{-\beta t} \cos(\omega_s t + \delta) \end{aligned}$$

START CLOCK AT
 $Q = Q_{\text{MAX}} = A_0$

FIND FREQUENCIES

$$\omega_N = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(0.01)(10 \times 10^{-6})}} = \underline{3162 \text{ s}^{-1}} = \omega_N$$

$$\beta = \frac{R}{2L} = \frac{10}{2(0.01)} = \underline{500 \text{ s}^{-1}} = \beta$$

$$\omega_s = \sqrt{\omega_N^2 - \beta^2} = \sqrt{(3162)^2 - (500)^2} = \underline{3122 \text{ s}^{-1}} = \omega_s$$

THE PERIODS ARE

$$T_N = \frac{2\pi}{\omega_N} = \frac{2\pi}{3162} = 1.987 \times 10^{-3} \text{ s} = \underline{1.99 \text{ ms}} = T_N$$

$$T_s = \frac{2\pi}{\omega_s} = \frac{2\pi}{3122} = 2.012 \times 10^{-3} \text{ s} = \underline{2.01 \text{ ms}} = T_s$$

AFTER TWO PERIODS

$$A(2T_s) = A_0 e^{-\beta t} = A_0 e^{-\beta(2T_s)} = A_0 e^{-2\beta T_s}$$

$$A_{2T_s} = A_0 e^{-2(500)(2.01)} = A_0 e^{-2.102}$$

$$\boxed{A_{2T_s} = 0.134 A_0}$$

So it's down to 13% after two periods!