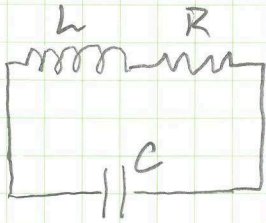


COMPUTE THE OSCILLATION FREQUENCIES, PERIODS AND AMPLITUDE AFTER 2 PERIODS (AS A FRACTION OF A_0) FOR THE CIRCUIT FOR $L = 0.01$, $C = 10 \mu\text{F}$ AND $R = 10 \Omega$.



KIRCHHOFF'S RULE GIVES

$$L\ddot{Q} + R\dot{Q} + \frac{1}{C}Q = 0$$

$$\Rightarrow \ddot{Q} + \frac{R}{L}\dot{Q} + \frac{1}{LC}Q = 0$$

FOR $\omega_N^2 = \frac{1}{LC}$ AND $2\beta = \frac{R}{L}$ THIS BECOMES

$$\ddot{Q} + 2\beta\dot{Q} + \omega_N^2 Q = 0$$

SO $Q(t) = A_0 e^{-\beta t} \cos(\omega_s t + \phi)$ ASSUME $\phi = 0$

$$I(t) = -A_0 e^{-\beta t} [\beta \cos(\omega_s t) + \omega_s \sin(\omega_s t)]$$

$$\text{WITH } \omega_N = \sqrt{\frac{1}{LC}} = \sqrt{\frac{1}{(0.01)(10 \times 10^{-6})}} = \boxed{3162.35 \text{ s}^{-1} = \omega_N}$$

$$\beta = \frac{R}{2L} = \frac{10}{2(0.01)} = \frac{100}{2} = \boxed{500 \text{ s}^{-1} = \beta}$$

$$\omega_s = \sqrt{\omega_N^2 - \beta^2} = \sqrt{(3162)^2 - (500)^2} = \boxed{3122 \text{ s}^{-1} = \omega_s}$$

$$T_s = \frac{2\pi}{\omega_s} = \frac{2\pi}{3122} = \boxed{2.01 \times 10^{-3} \text{ SEC} = T_s}$$

AT $2T_s = 4.02 \times 10^{-3} \text{ S}$, FIND THE AMPLITUDE

$$A(t = 2T_s) = A_0 e^{-\beta(2T_s)} = A_0 e^{-(500)(4.02 \times 10^{-3})}$$

$$\boxed{A(t = 2T_s) = 0.13369 A_0}$$

$$\rightarrow \nu_0 = \frac{\omega_s}{2\pi} = 4.967 \text{ kHz}$$

$$\rightarrow \nu_N = \frac{\omega_N}{2\pi} = 4.904 \text{ kHz}$$

NOT STRONG DAMPING