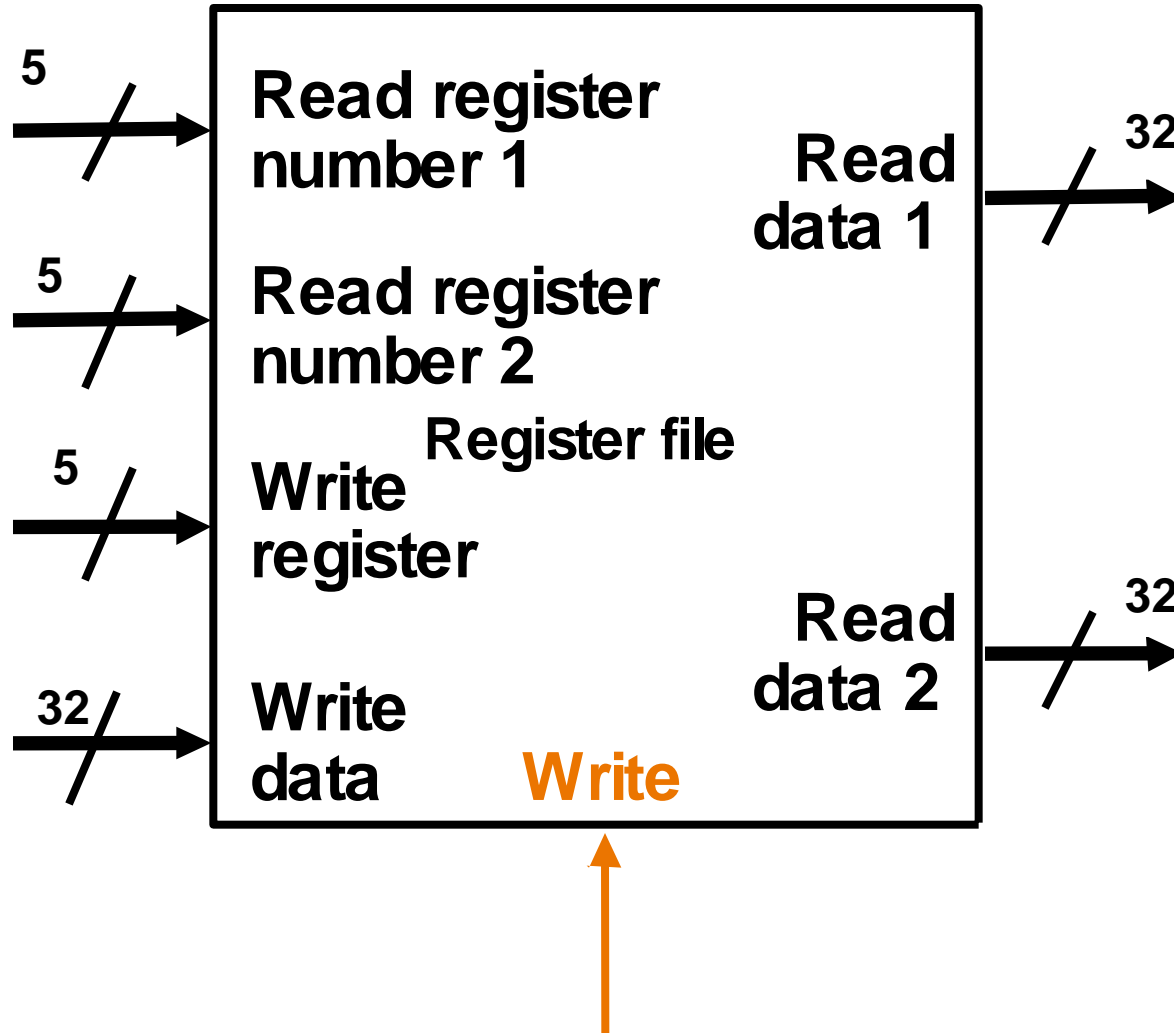



CS 220

The Processor
Single Cycle Datapath
4.1 – 4.4


Register Files





Register Files: The Read Ports

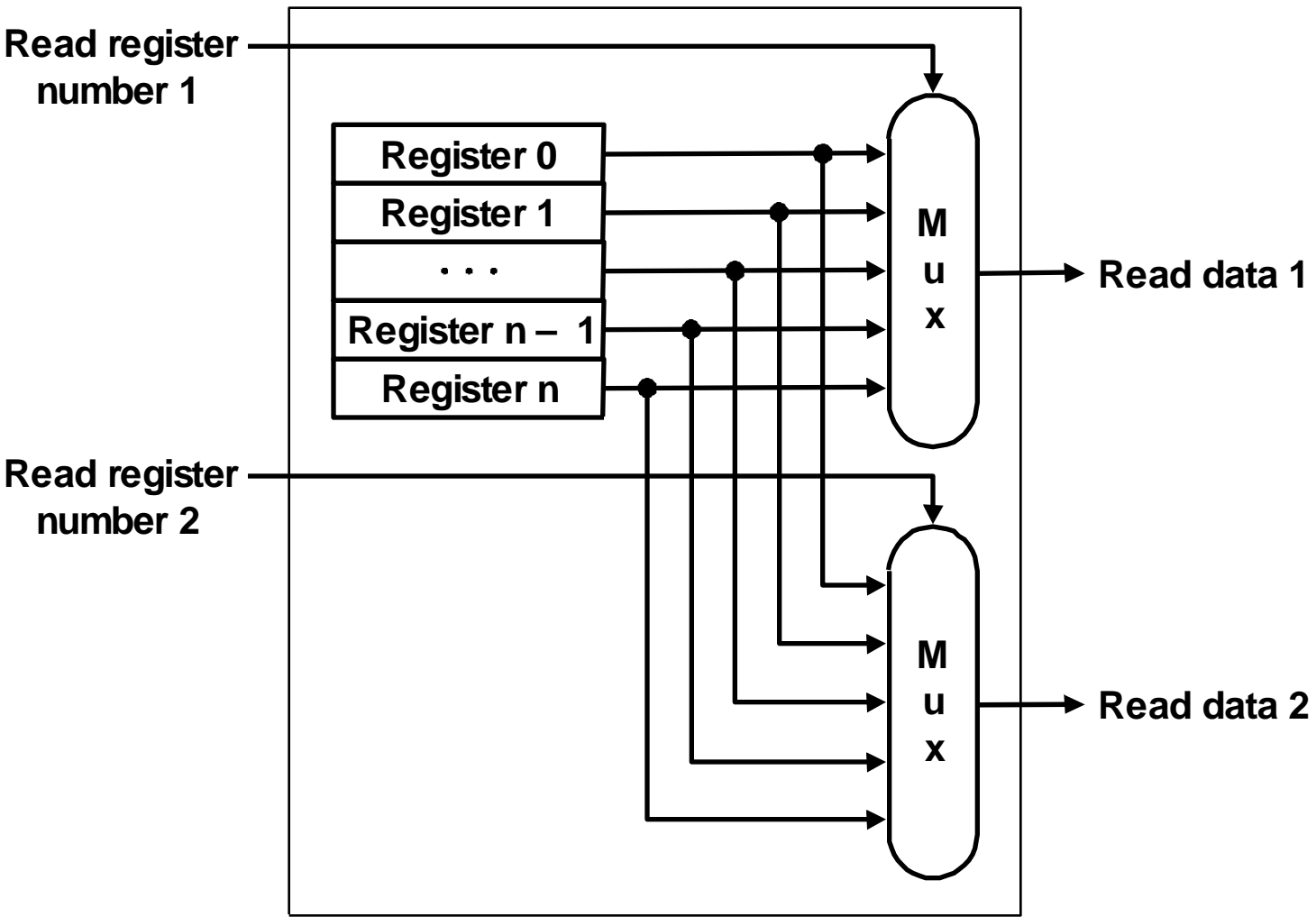

Register Files: The Write Port

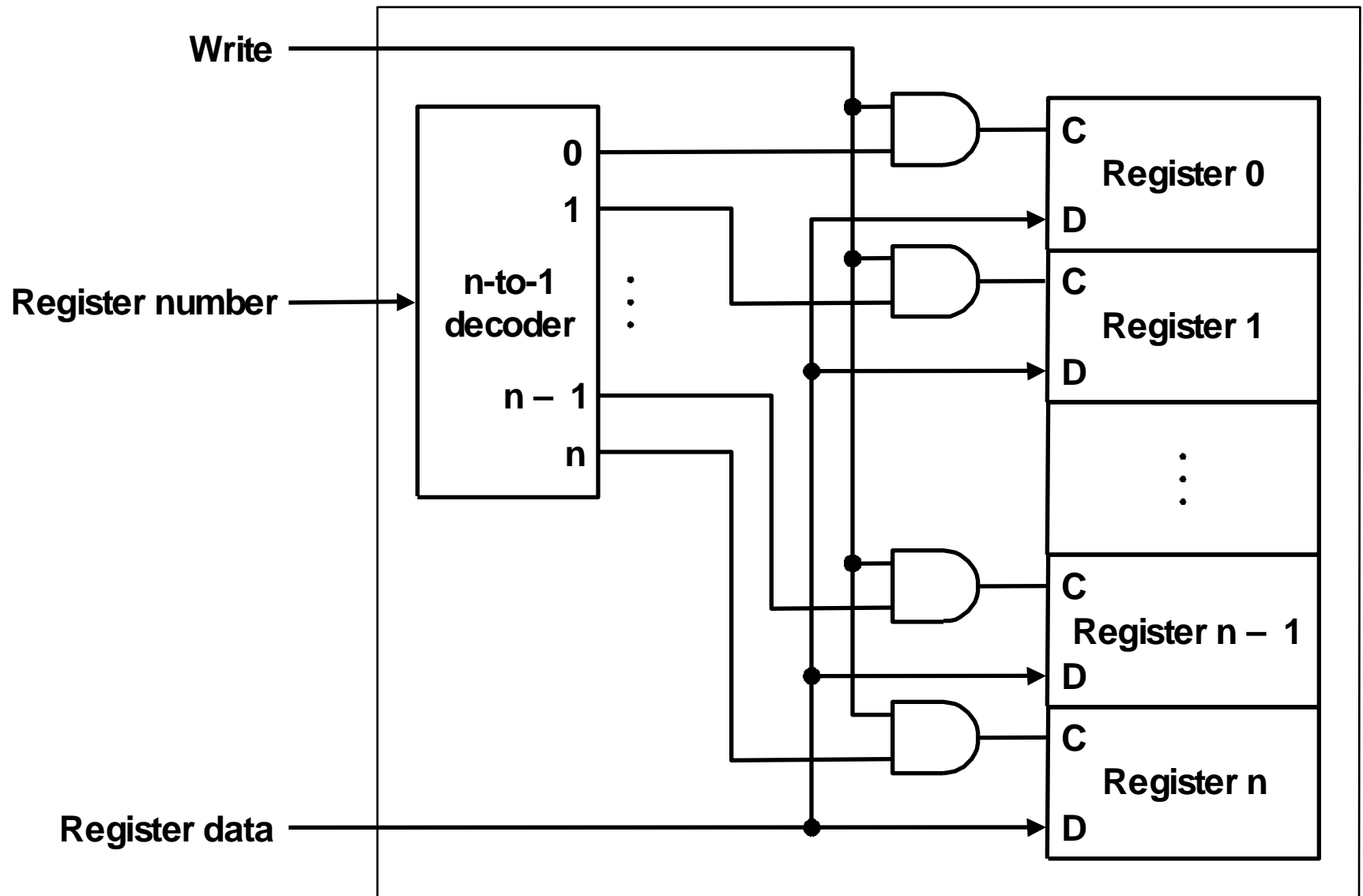


Register Files

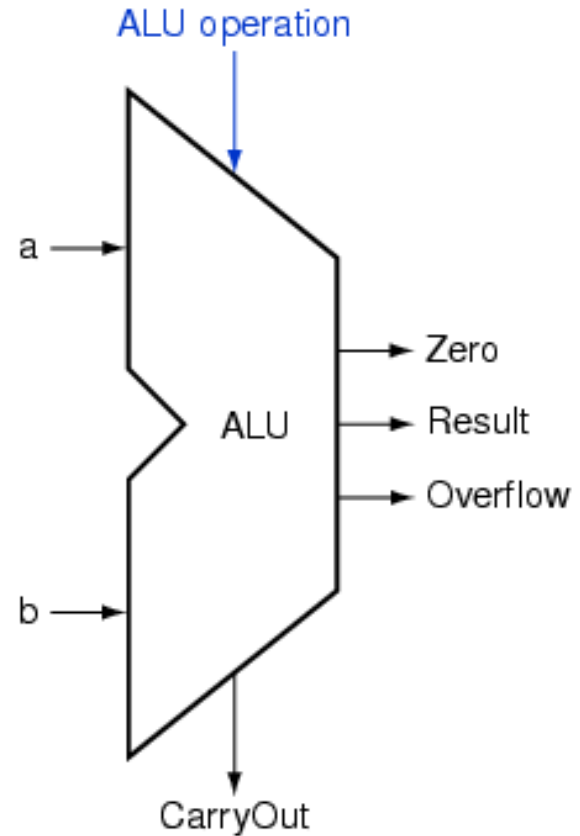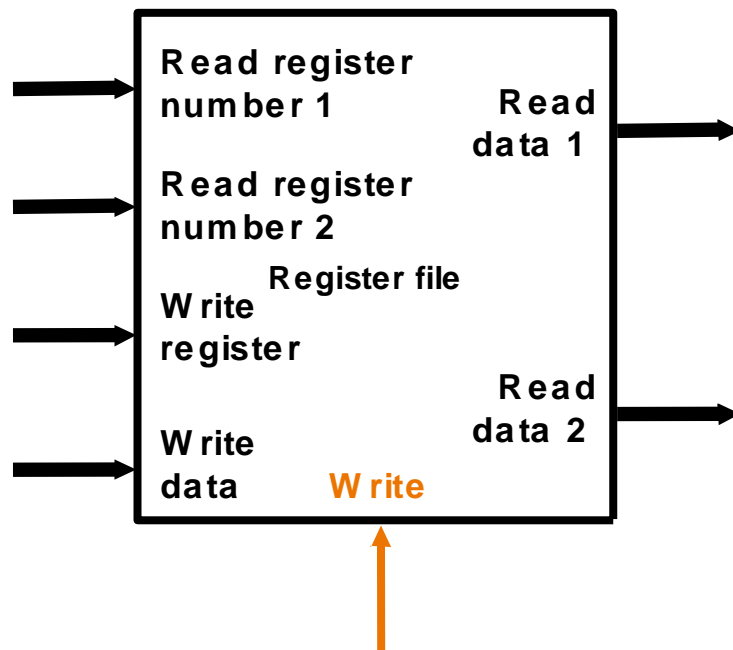


Sequential Logic



 
- Usually use edge triggered timing
- Changes appear on the rising or falling edge.
 - Assume changes ready on next rising edge



Sequential Logic

 - Can the same **state element** be read and written at the same time?
- `add $t0, $t0, $t0`




  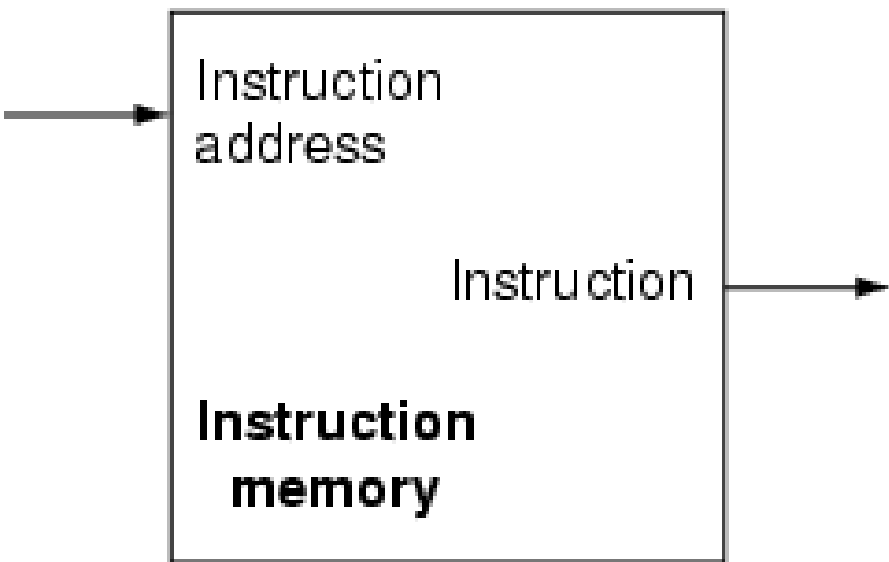


MIPS Subset

- Memory instructions lw/sw
 - `lw $t0, 4($sp)`
- Simple arithmetic add, sub, slt, ...
 - `add $t0, $t1, $t2`
 - `addi $t0, $t1, 234`
- Branches beq, j
 - `beq $zero, $s0, offset`
 - `j address`


Abstract View of MIPS processor

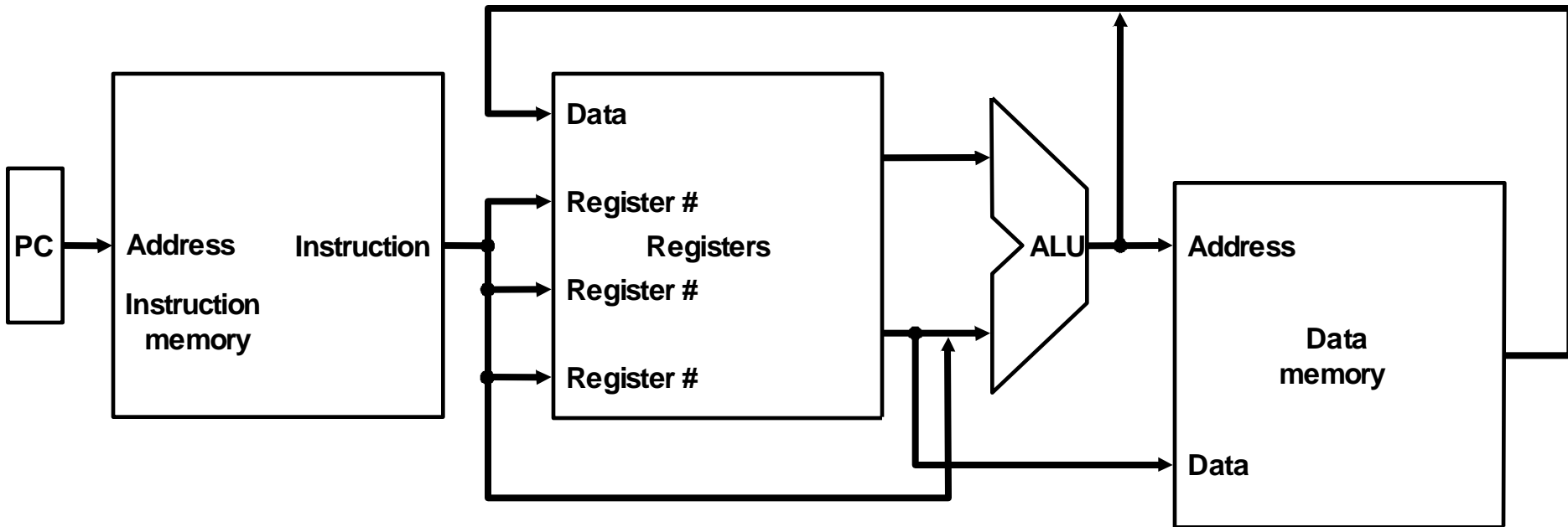


Fetching instruction from Memory

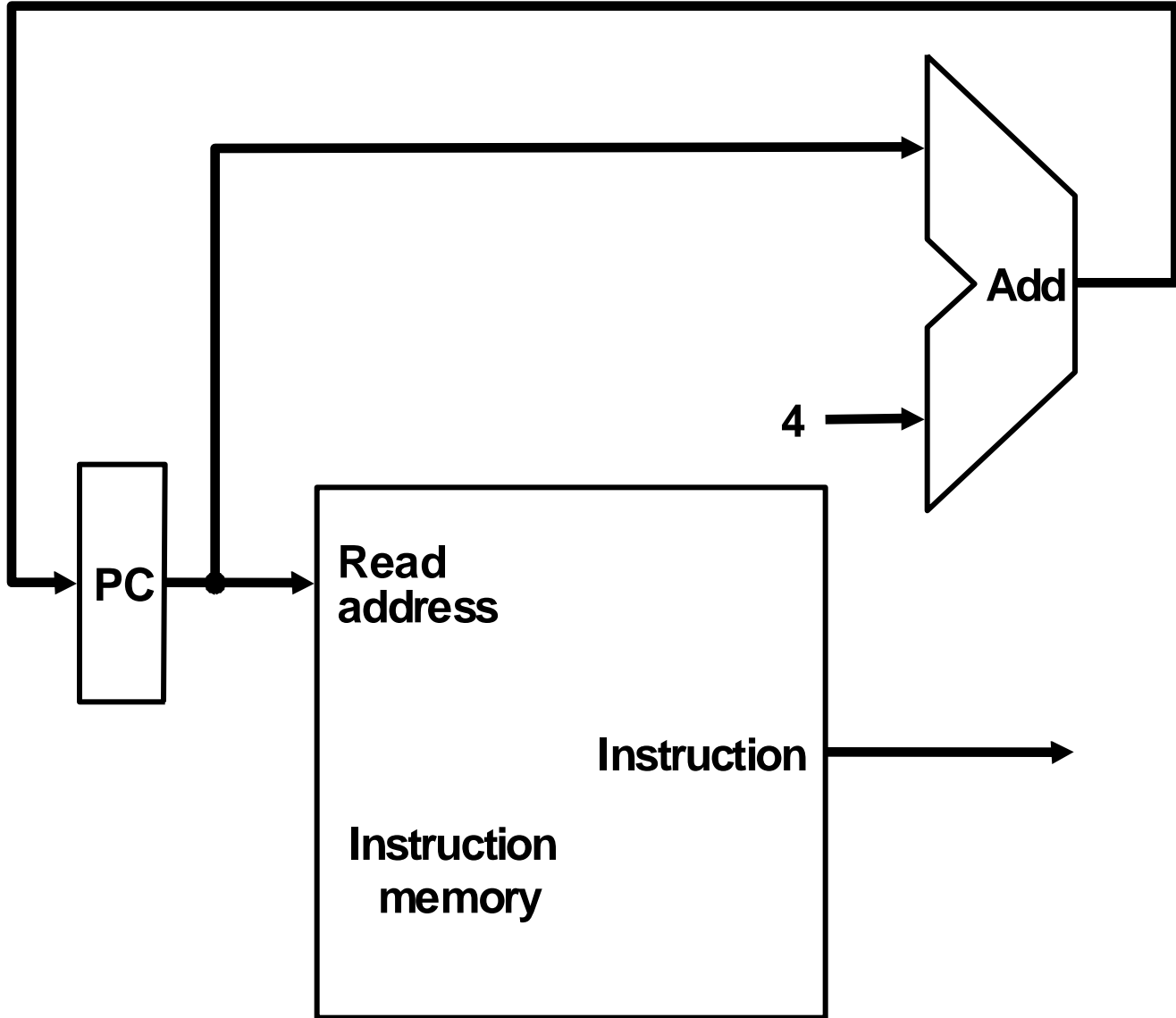

Recall the MIPS Registers

 


Executing R-Type Instructions

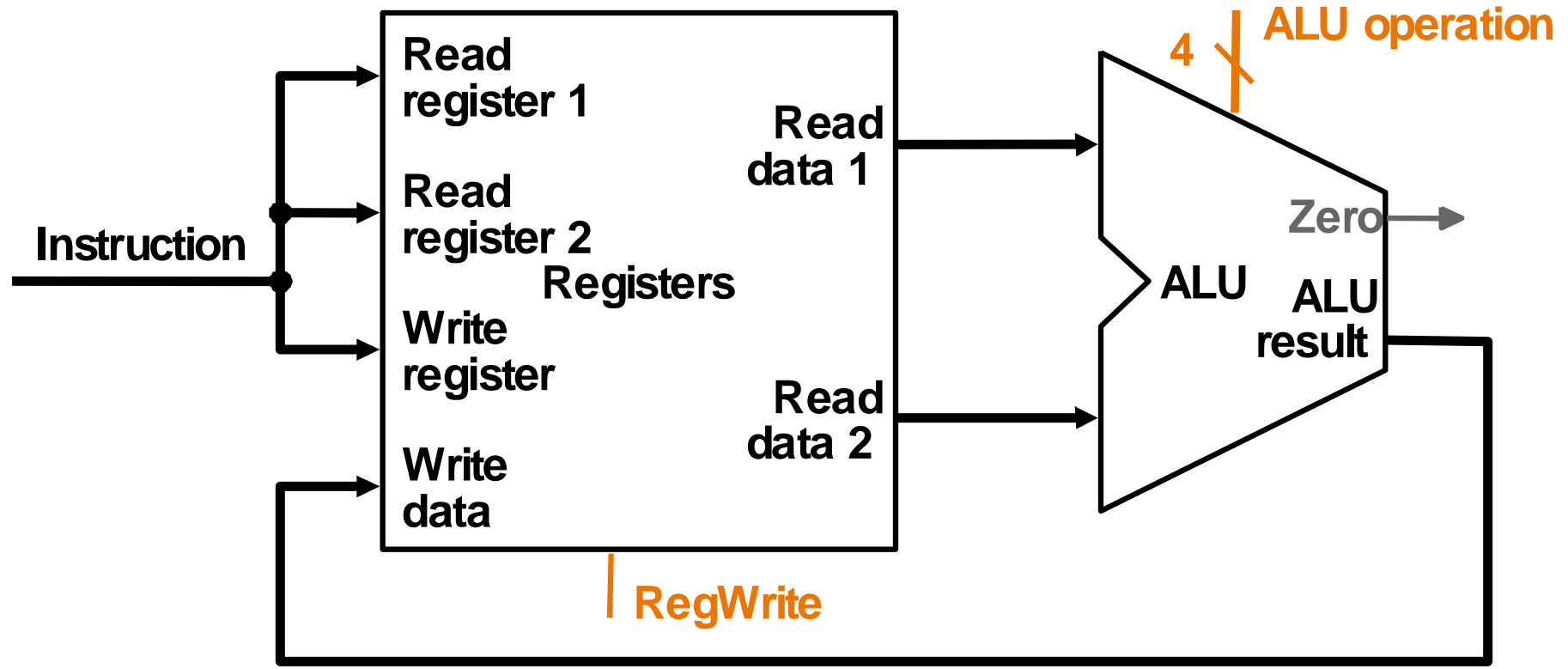


Executing Load/Store instructions

- A load/store does a
 1. register access then
 2. a memory address calculation
 3. read or write from memory
- Load/Store Instruction format is an I-format
 - `lw $1, 100($2)`
 - 16 bit signed offset is added to register

Load/Store Instructions

 


a. Data memory unit

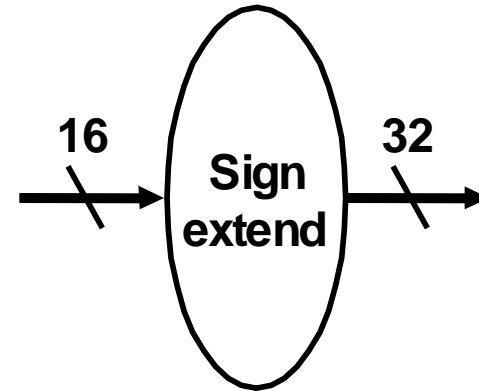

b. Sign-extension unit

Datapath for Load/Store Instructions

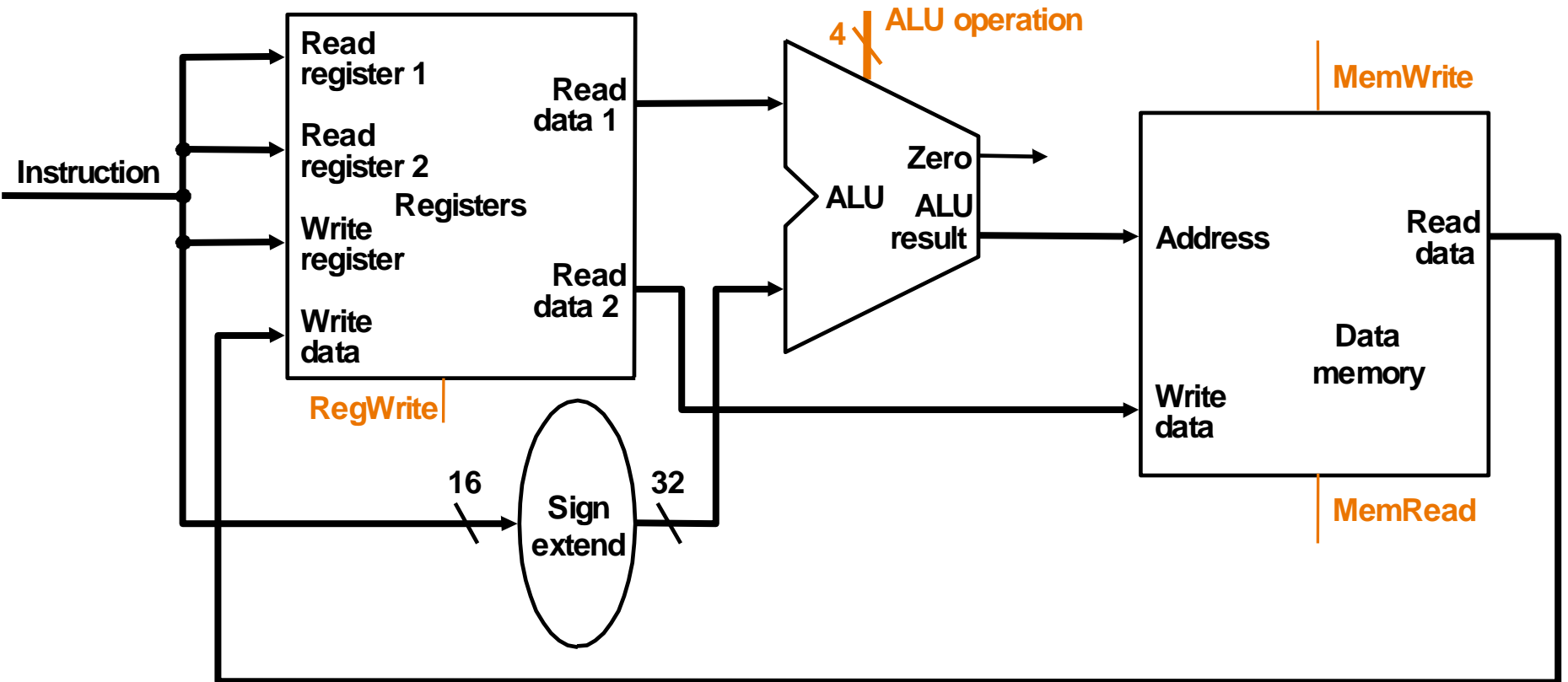


PC-relative addressing

```
loop: addi $s0, $s0, -1  
      bne $s0, $zero, loop
```

Gets translated to

```
loop: addi $16, $16, -1  
      bne $16, $0, _____
```


Datapath for branch instructions

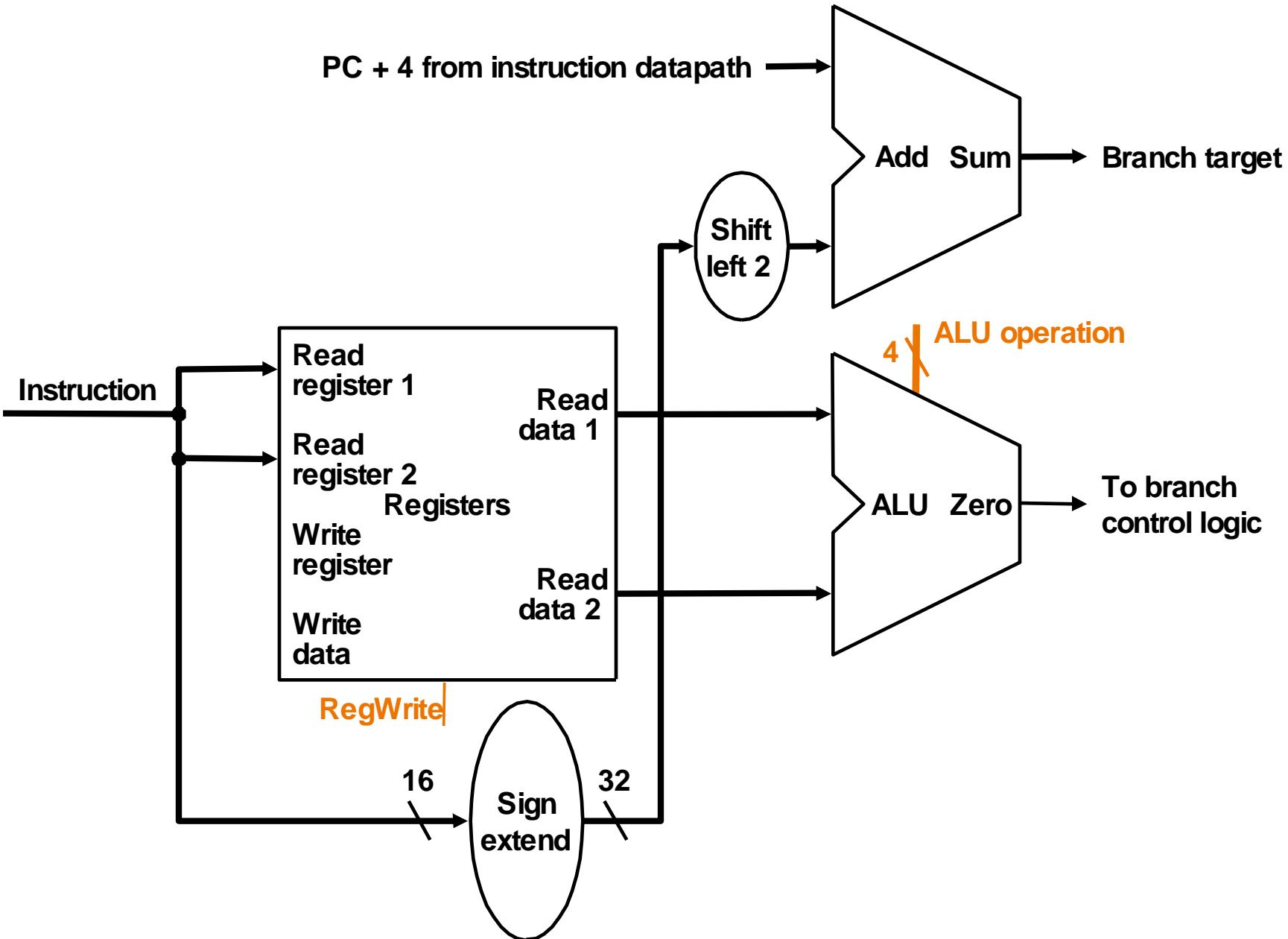


Combining Datapaths

- We have built datapaths for
 - R-type instructions
 - and Some I-type instructions
 - lw/sw instructions
 - beq
- Need to combine these
 - into a single datapath
 - allows us to reuse registers, ALU, etc.


Combining Datapaths (R and lw/sw)

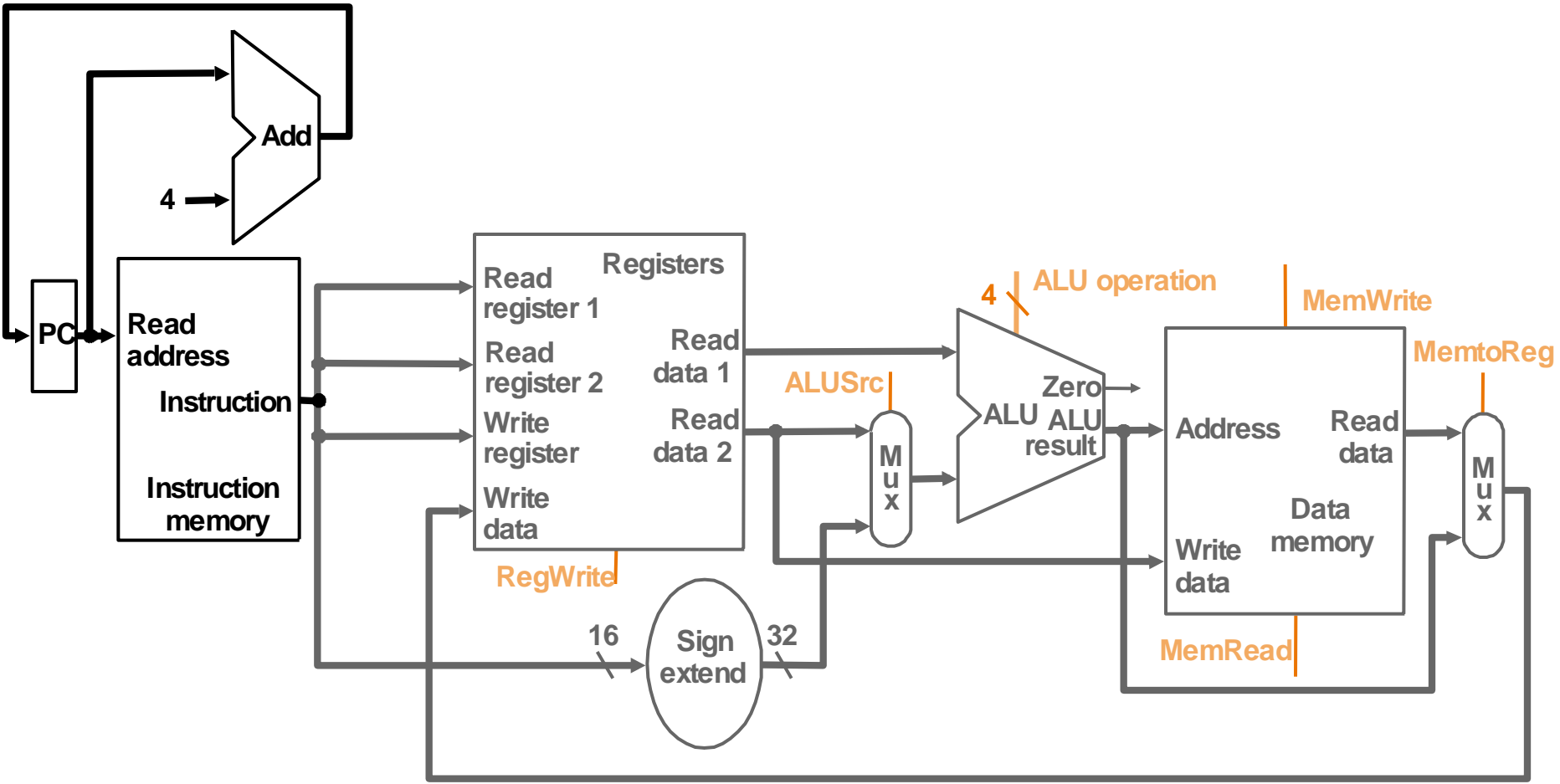

R type + lw/sw + branch

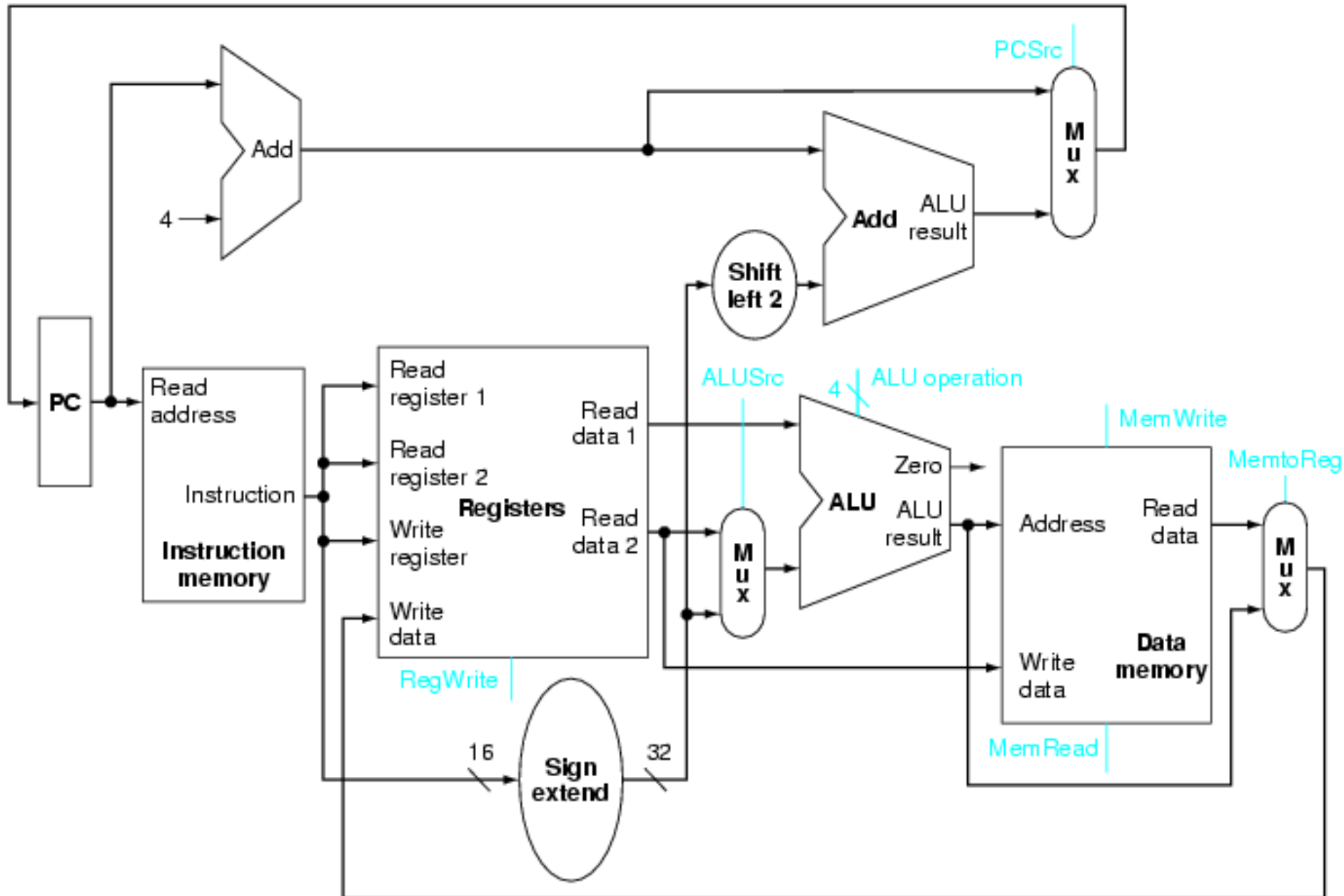

Controlling the ALU (page 316)

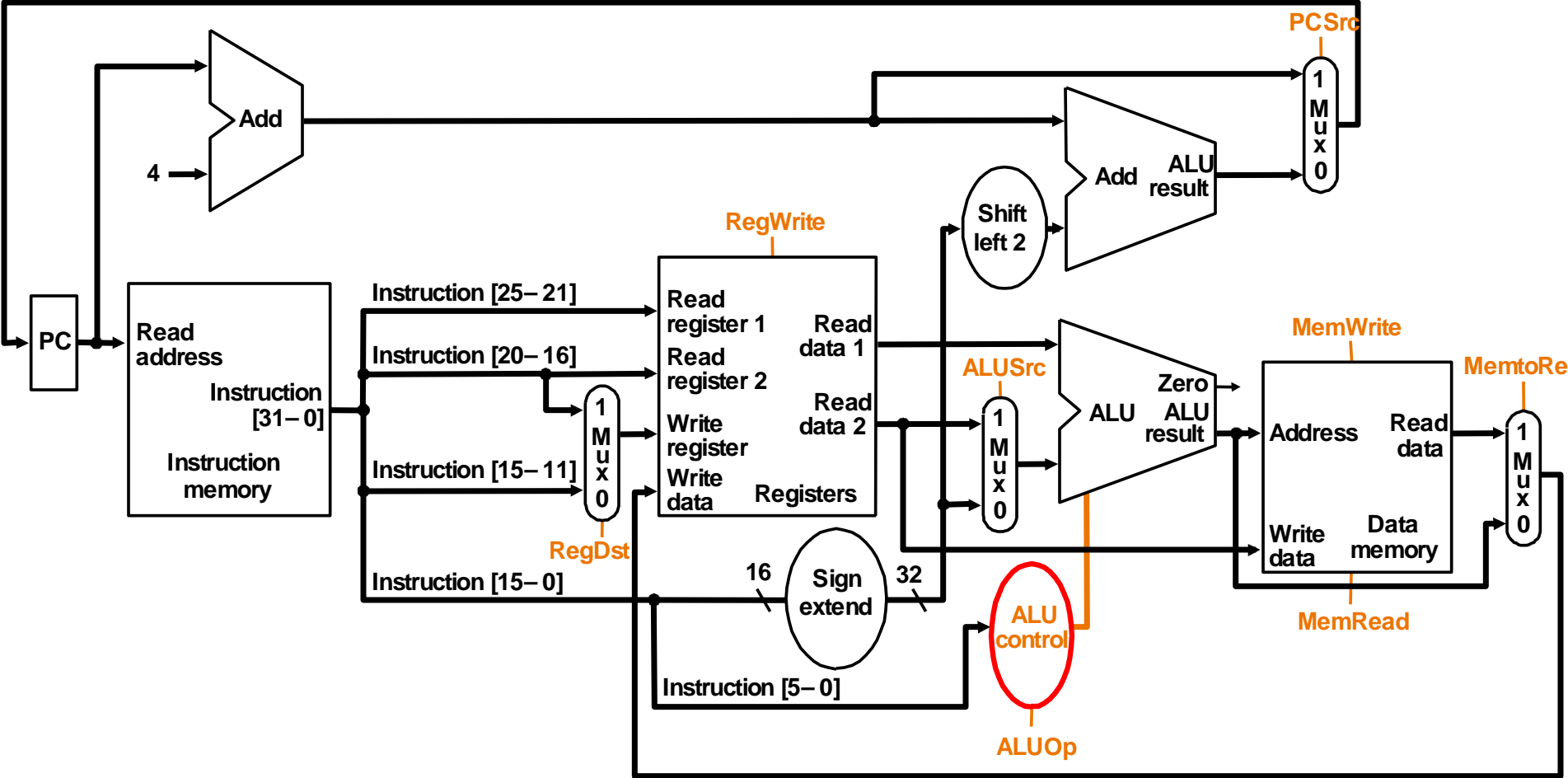

ALU Control (page 316)

- AND 0000
- OR 0001
- add 0010
- subtract 0110
- set on less than 0111
- NOR 1100

Controlling the ALU


Opcode	ALUop	Operation	Funct field	ALU Action	ALU Control
lw	00	lw	X		
sw	00	sw	X		
beq	01	beq	X		
R	10	Add	100000		
R	10	Sub	100010		
R	10	And	100100		
R	10	Or	100101		
R	10	Slt	101010		

Controlling the ALU: truth table


ALUop		Funct Field						ALU Operation			
Op ₁	Op ₀	f ₅	f ₄	f ₃	f ₂	f ₁	f ₀	ALU ₃	ALU ₂	ALU ₁	ALU ₀
0	0	x	x	x	x	x	x	0	0	1	0
0	1	x	x	x	x	x	x	0	1	1	0
1	0	x	x	0	0	0	0	0	0	1	0
1	0	x	x	0	0	1	0	0	1	1	0
1	0	x	x	0	1	0	0	0	0	0	0
1	0	x	x	0	1	0	1	0	0	0	1
1	0	x	x	1	0	1	0	0	1	1	1

The Main Control Unit

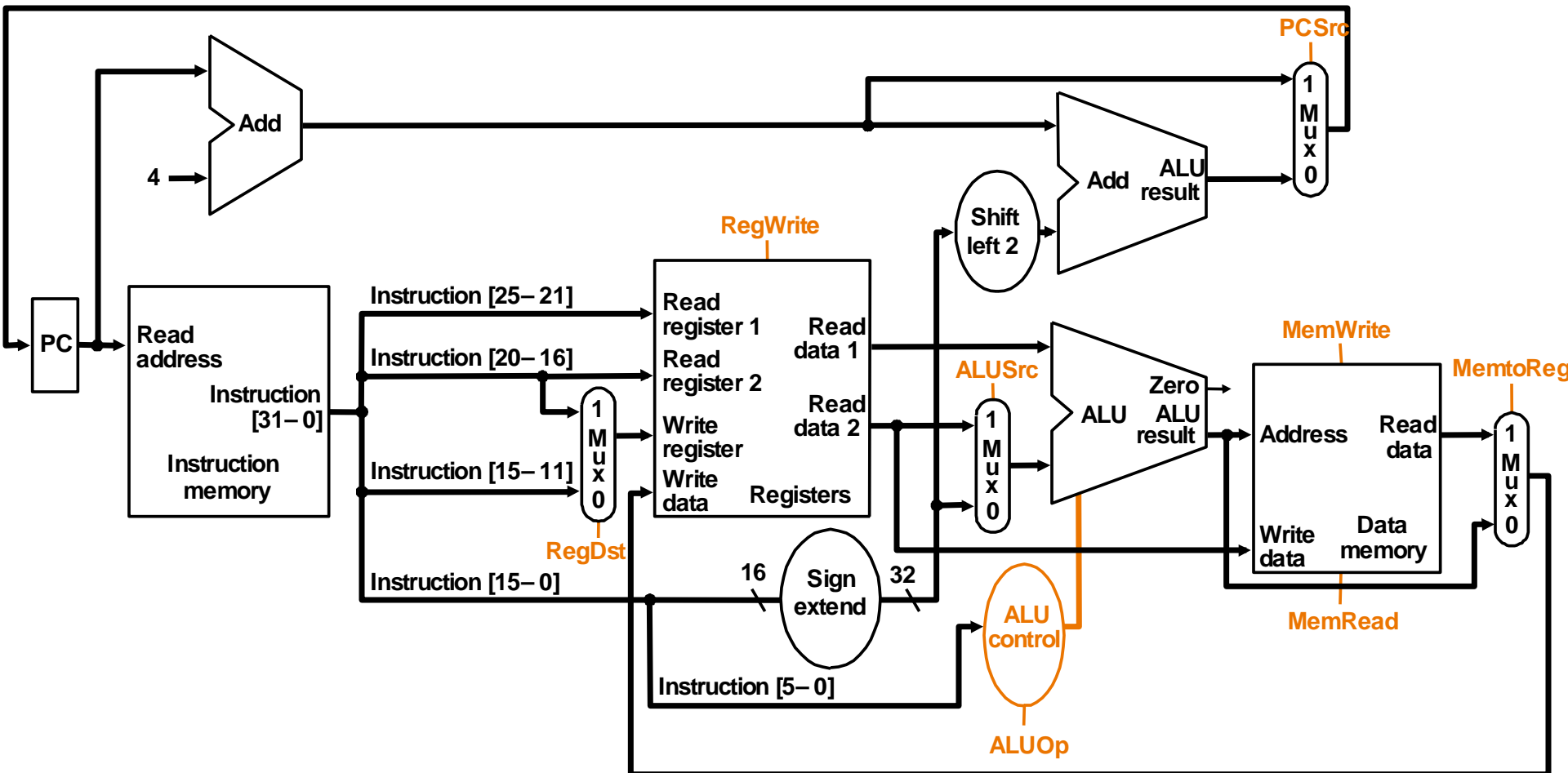We are left with 9 control signals that need to be set to 0 or 1 on the basis of 6 remaining opcode bits.



The Main Control Unit

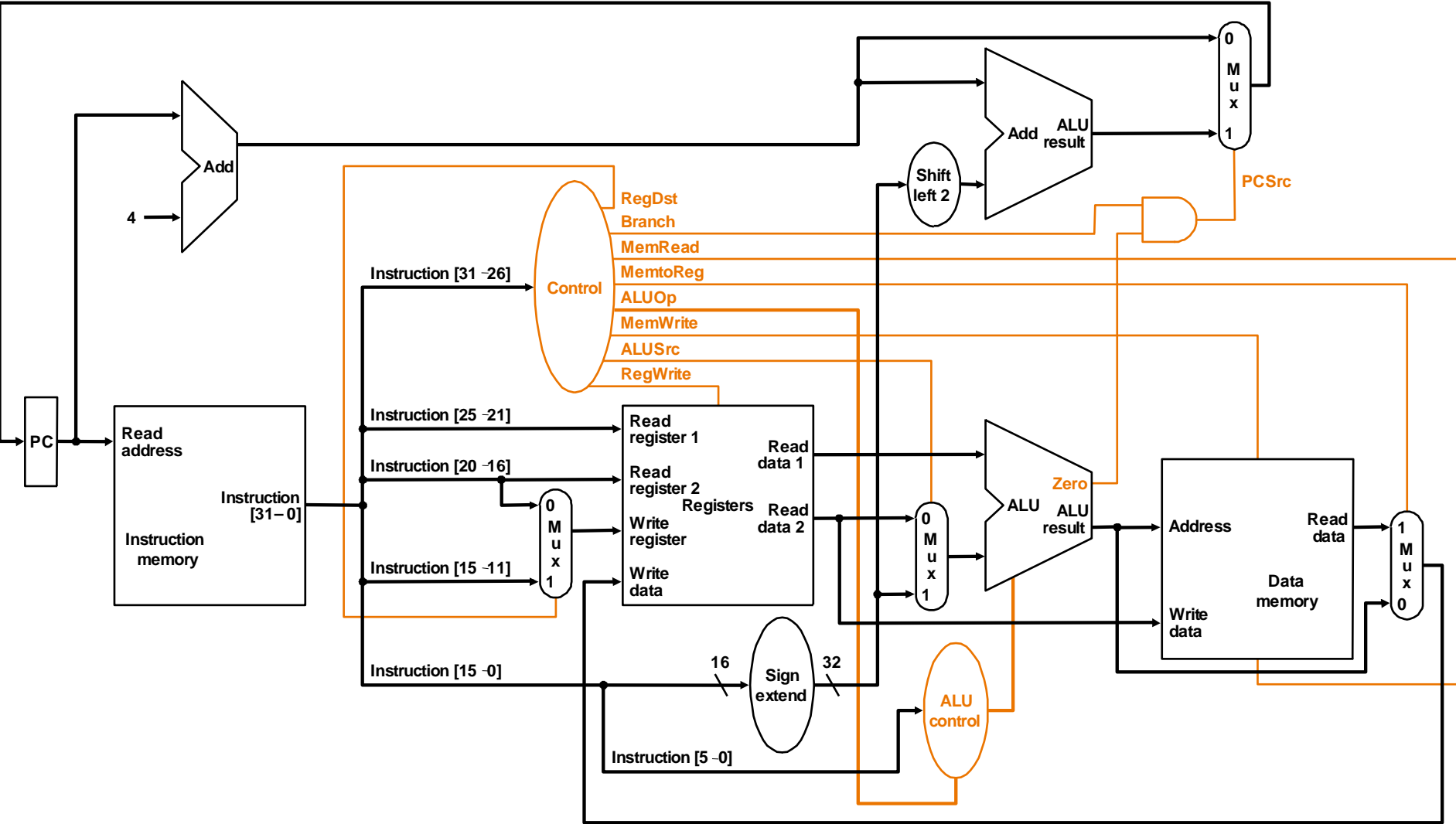

Designing the Main Control Unit

- What are the different opcodes we are supporting?
- See table page 308

Ins	Reg Dst	ALU Src	MemtoReg	Reg Write	Mem Read	Mem Write	Branch	ALUOp1	ALUOp0
R									
lw									
sw									
beq									

Can we write the logic equations?