


For two 32-bit quantities **a** and **b**.


What are the settings to compute:

- **a + b**
- **a - b**
- **a < b**
- **a or b**
- **a and b**
- **a nor b**
- **a nand b**

Trace on $2 < 3$


```
li $t0, 2  
slti $t1, $t0, 3
```

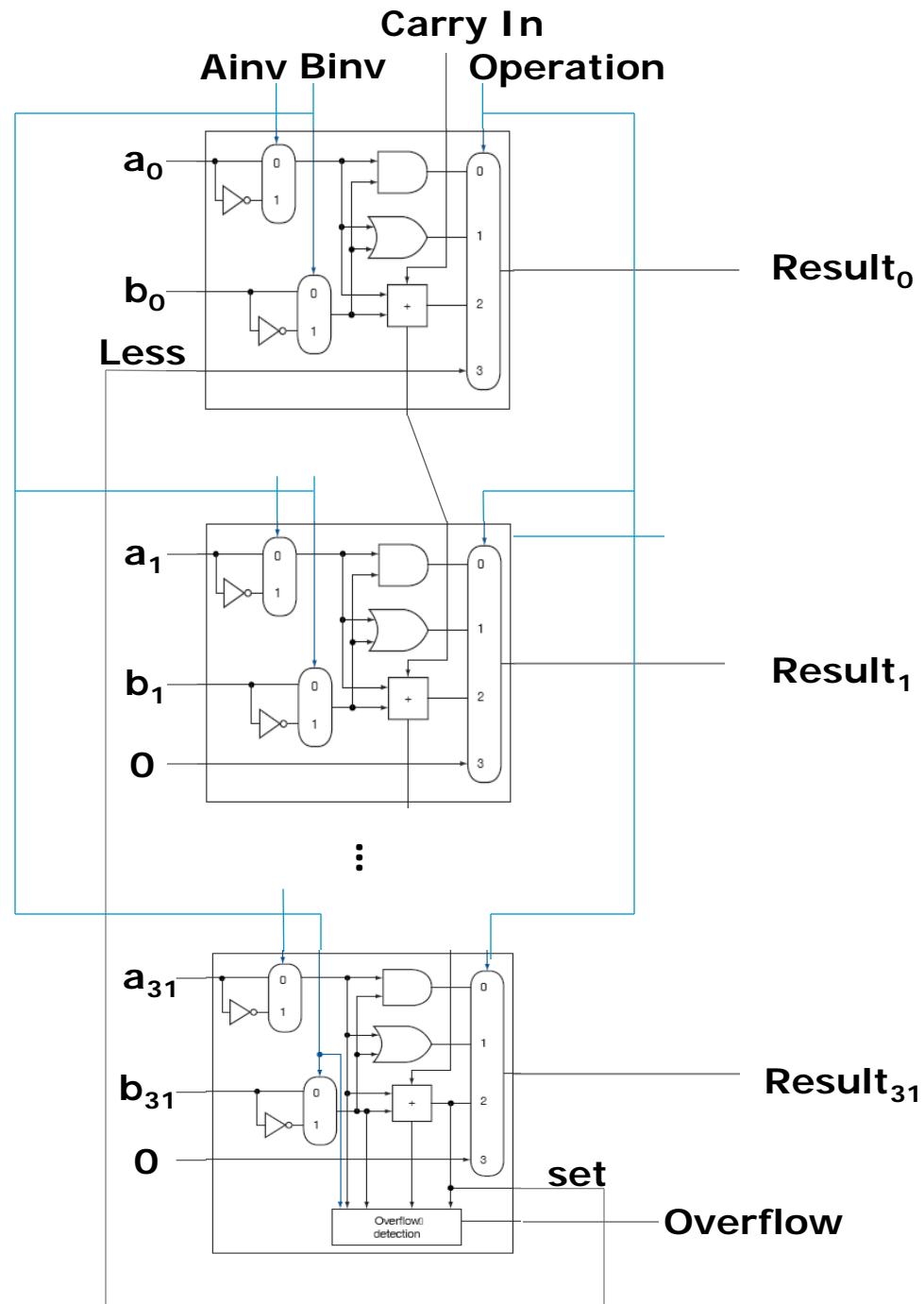

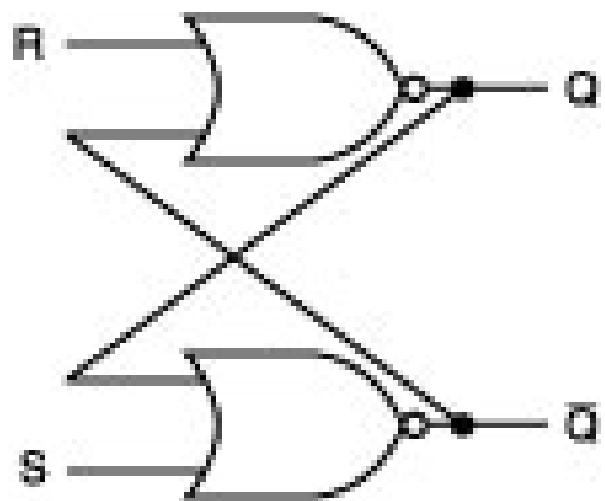

S-R Latch

Write Enable

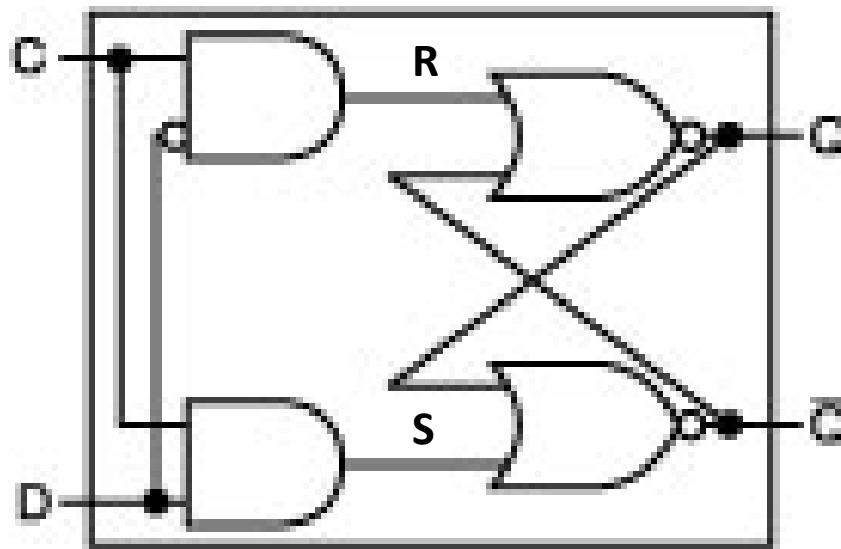

D Latch



(Page C-52)

Q