

CS 220

The MIPS Instruction Pipeline – Part 2

Reading memory

Analyze a data dependency with a **lw** instruction.

```
lw t0, 0(sp)  
add t1, t0, t0
```


Solutions?


Can we minimize stalling?

$A = B + E$


$C = B + F$

Assuming these variables are stored in memory write the MIPS code for these statements.


Pipelined Datapath

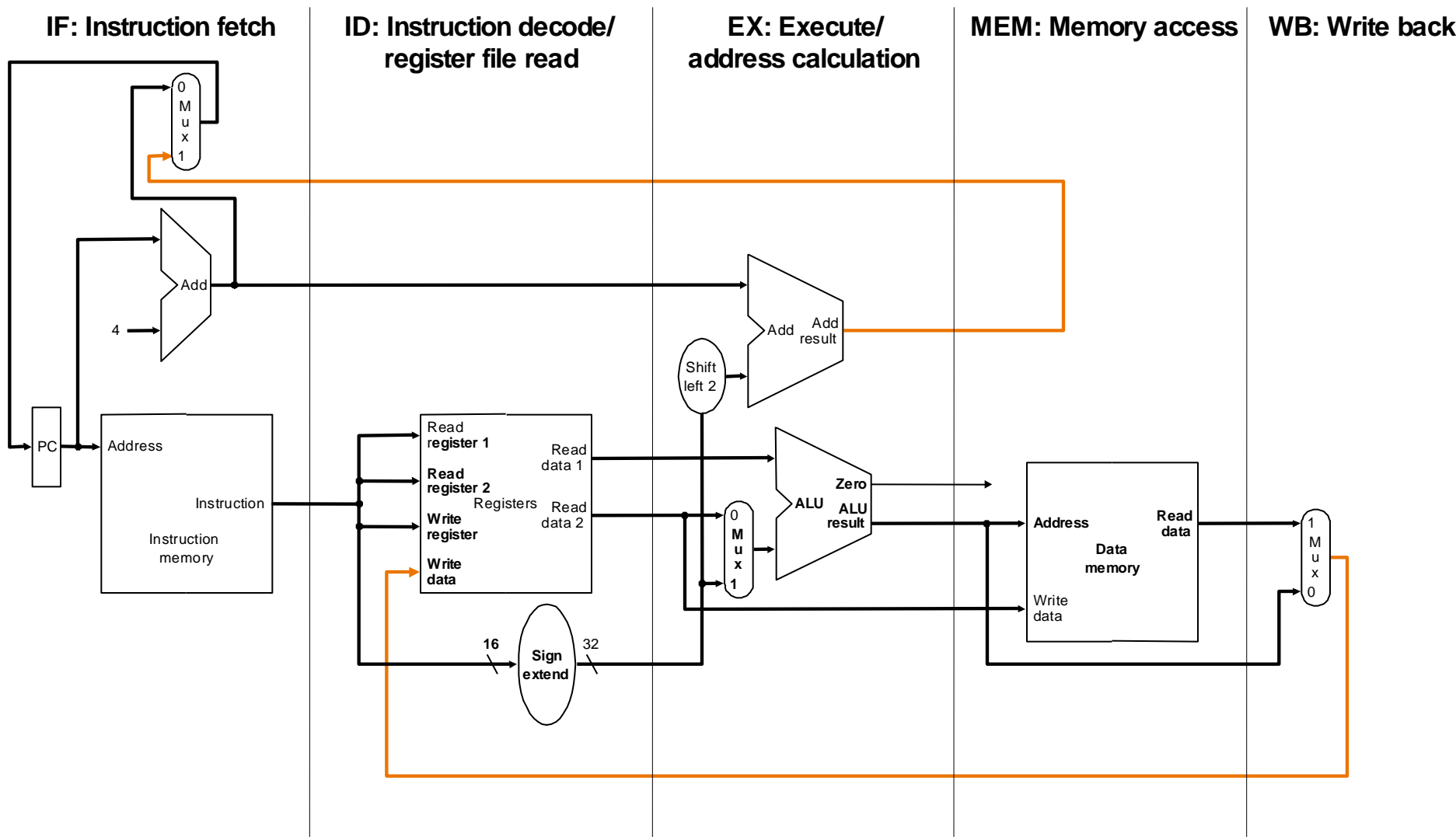


Pipelined Datapath

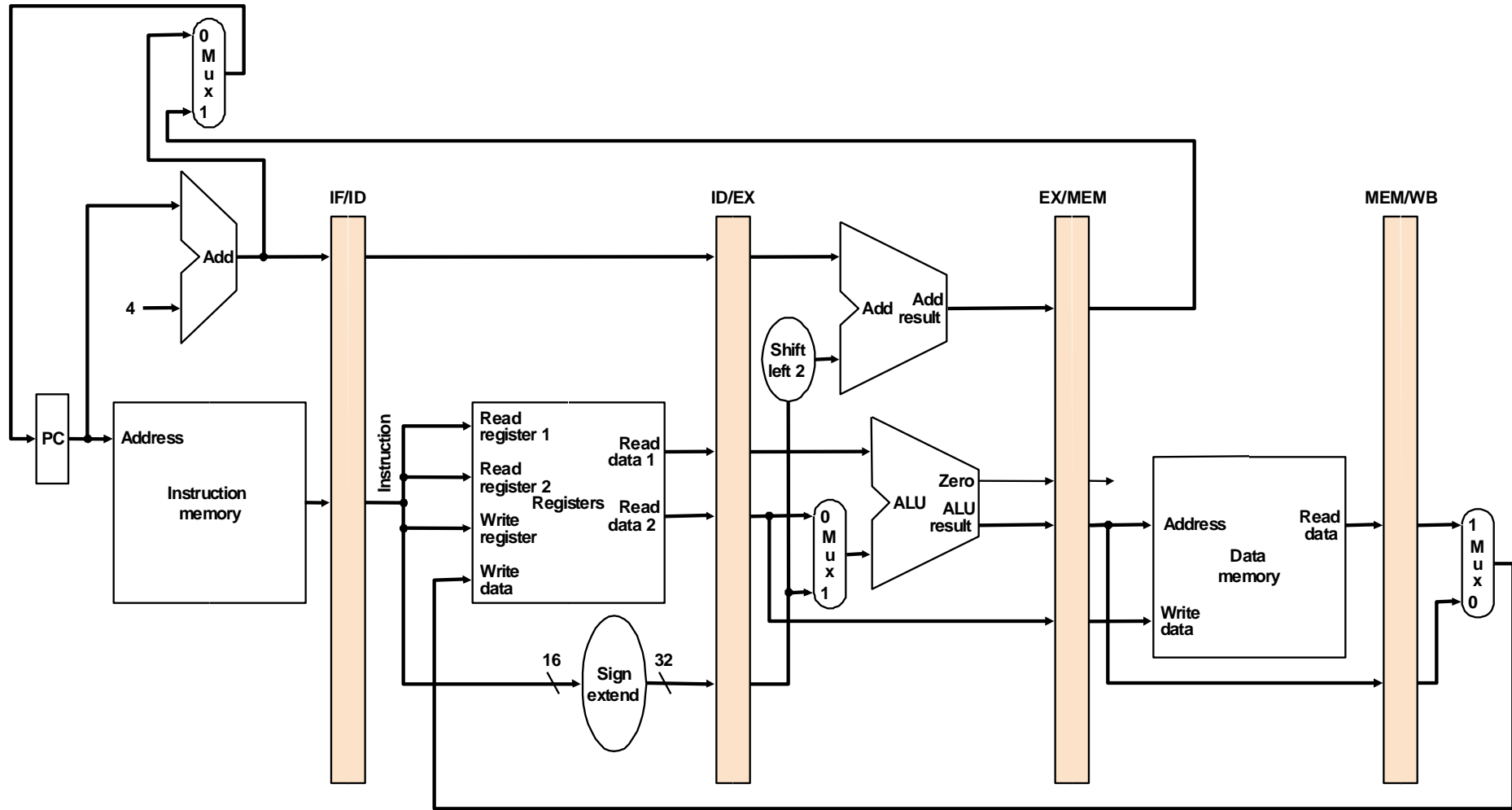


Tracing a LW instruction

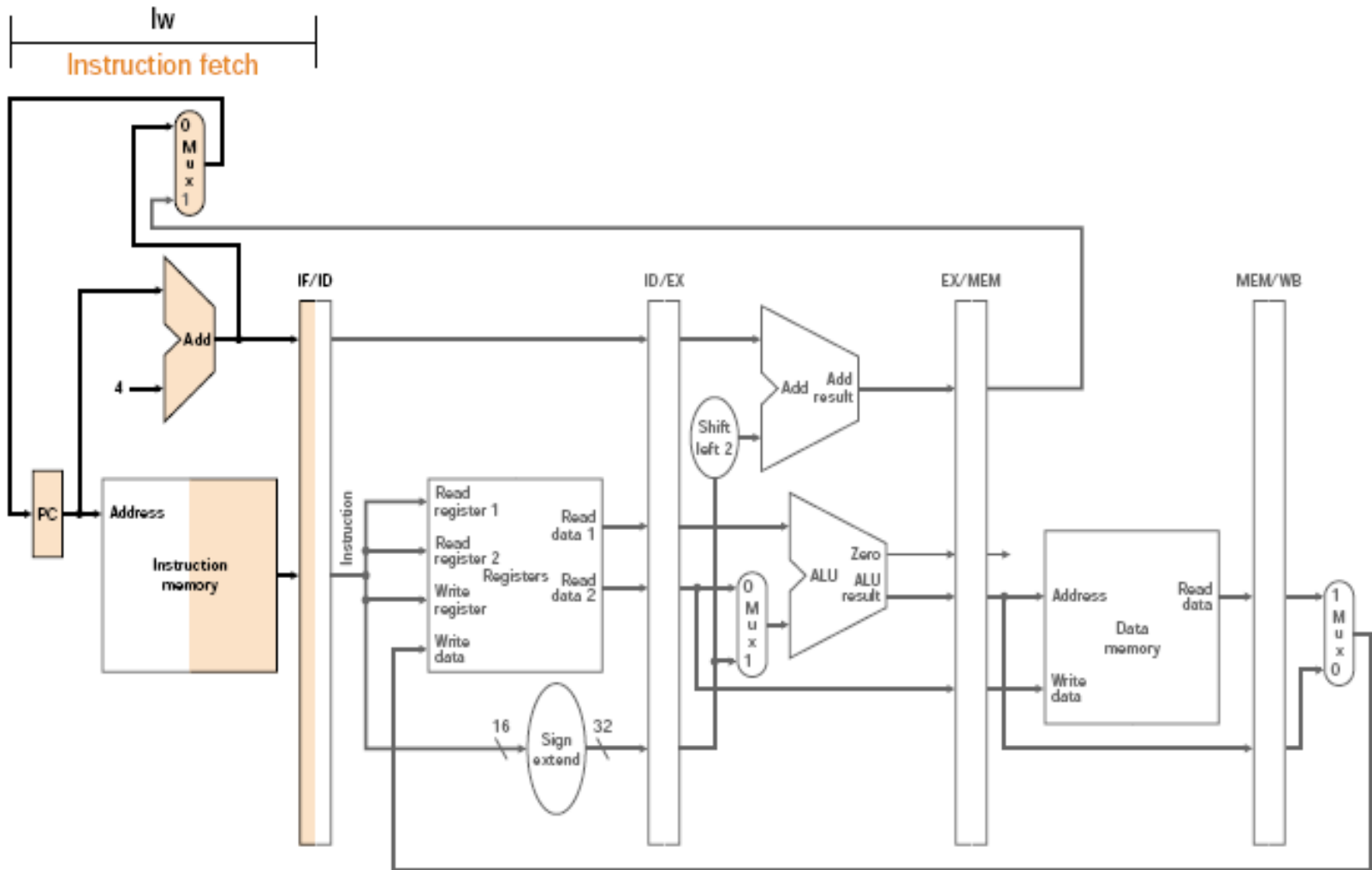


Tracing a LW instruction

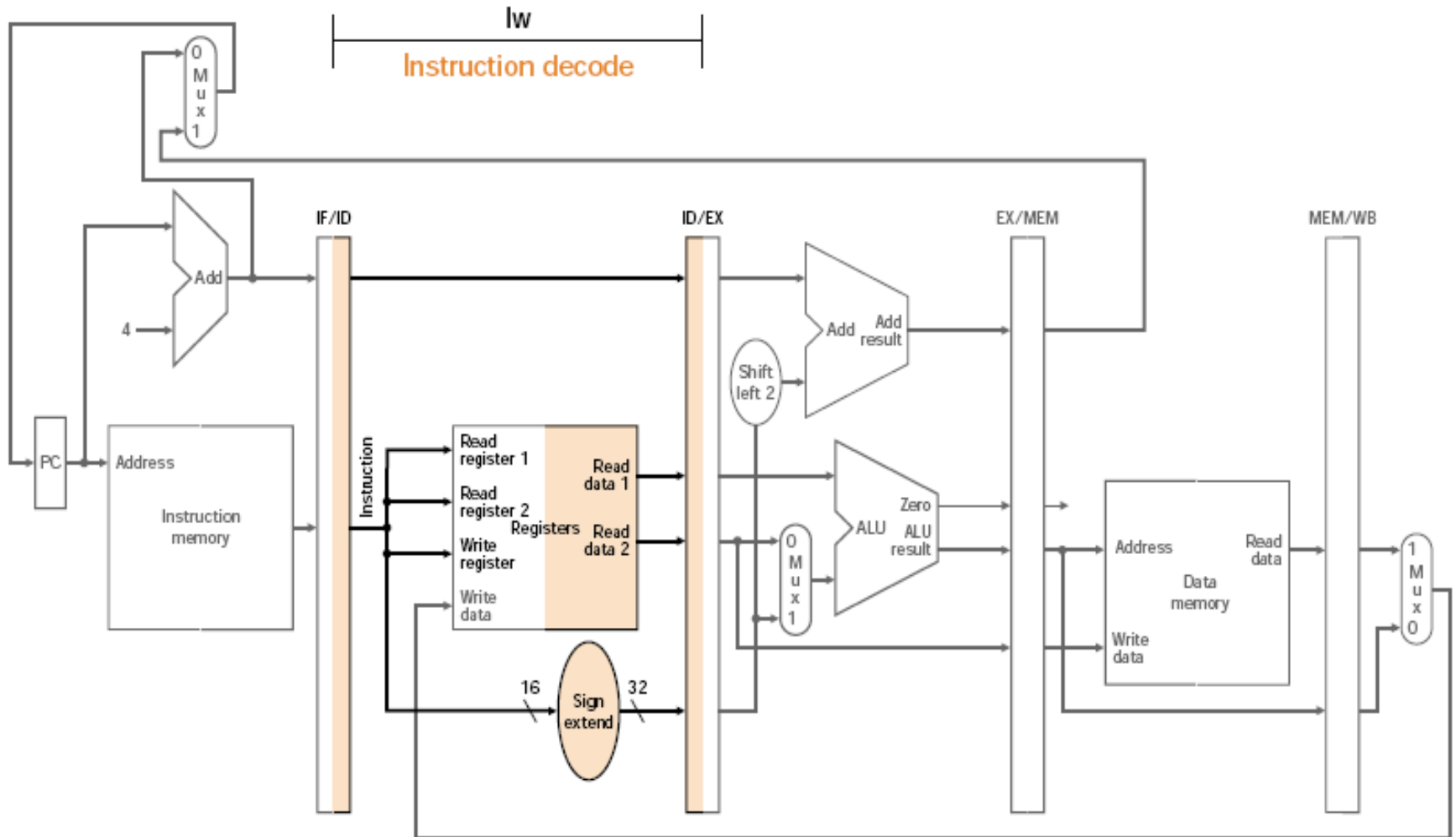


Tracing LW: EX

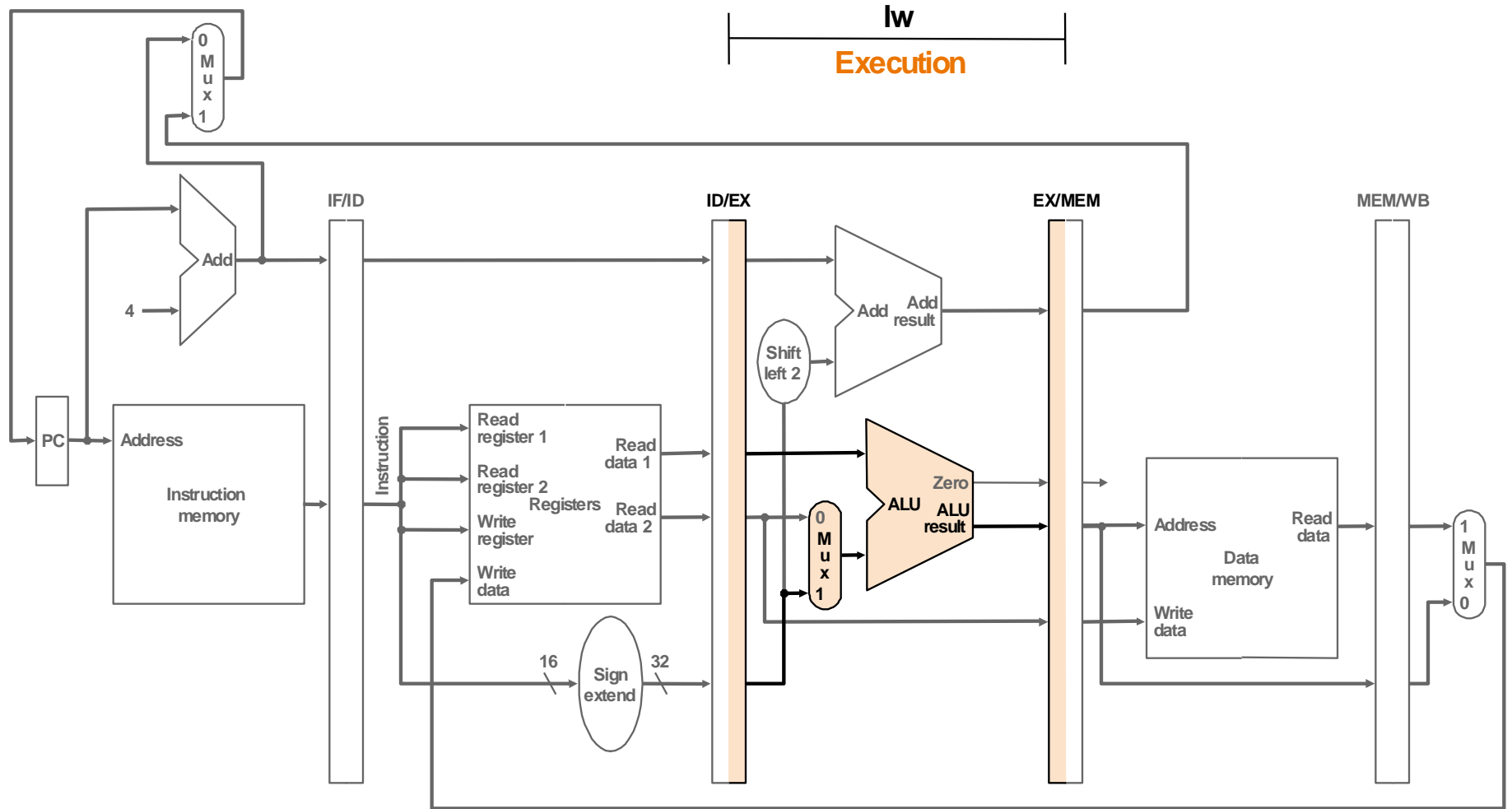

LW: Memory

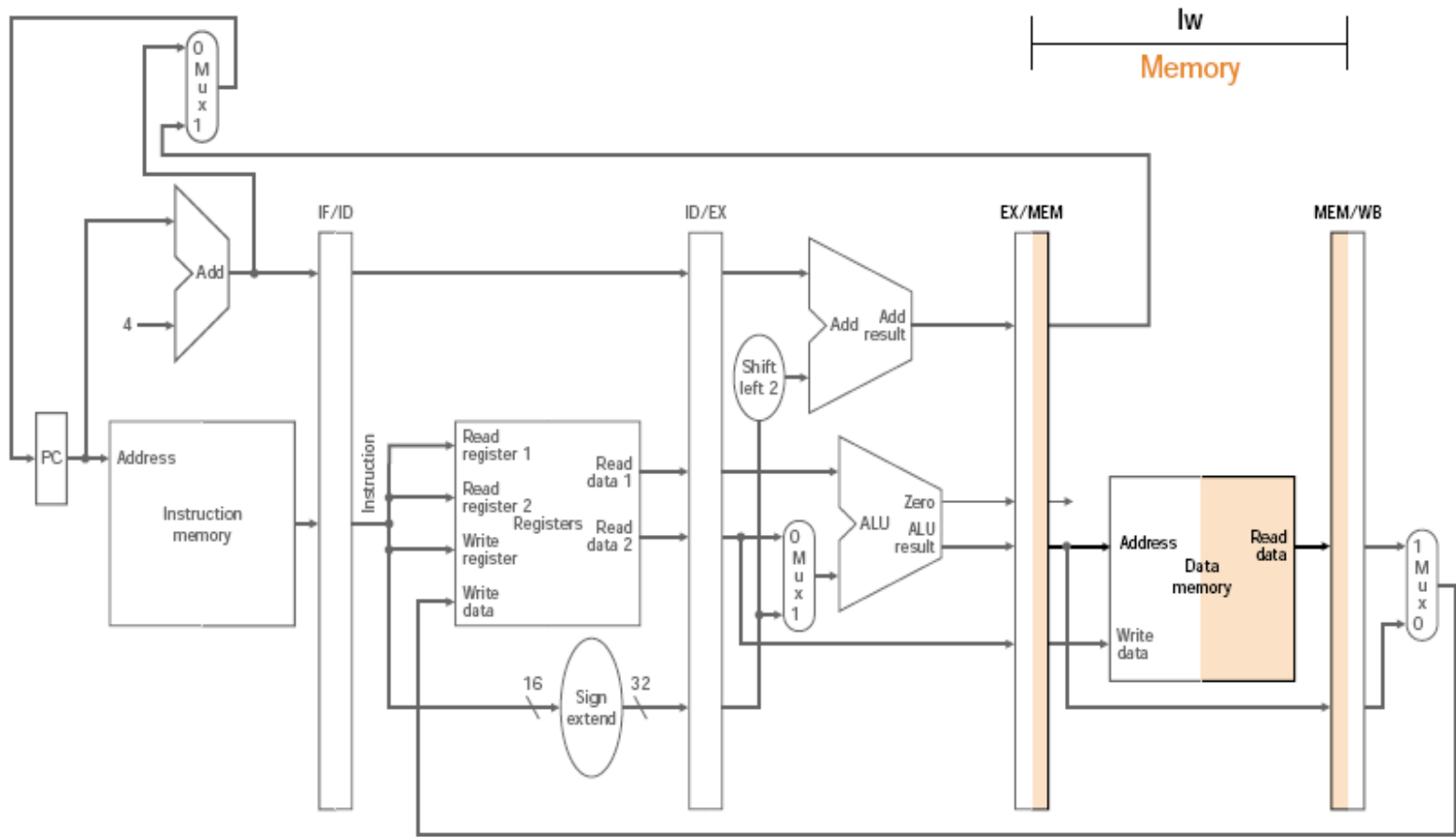


LW: Writeback

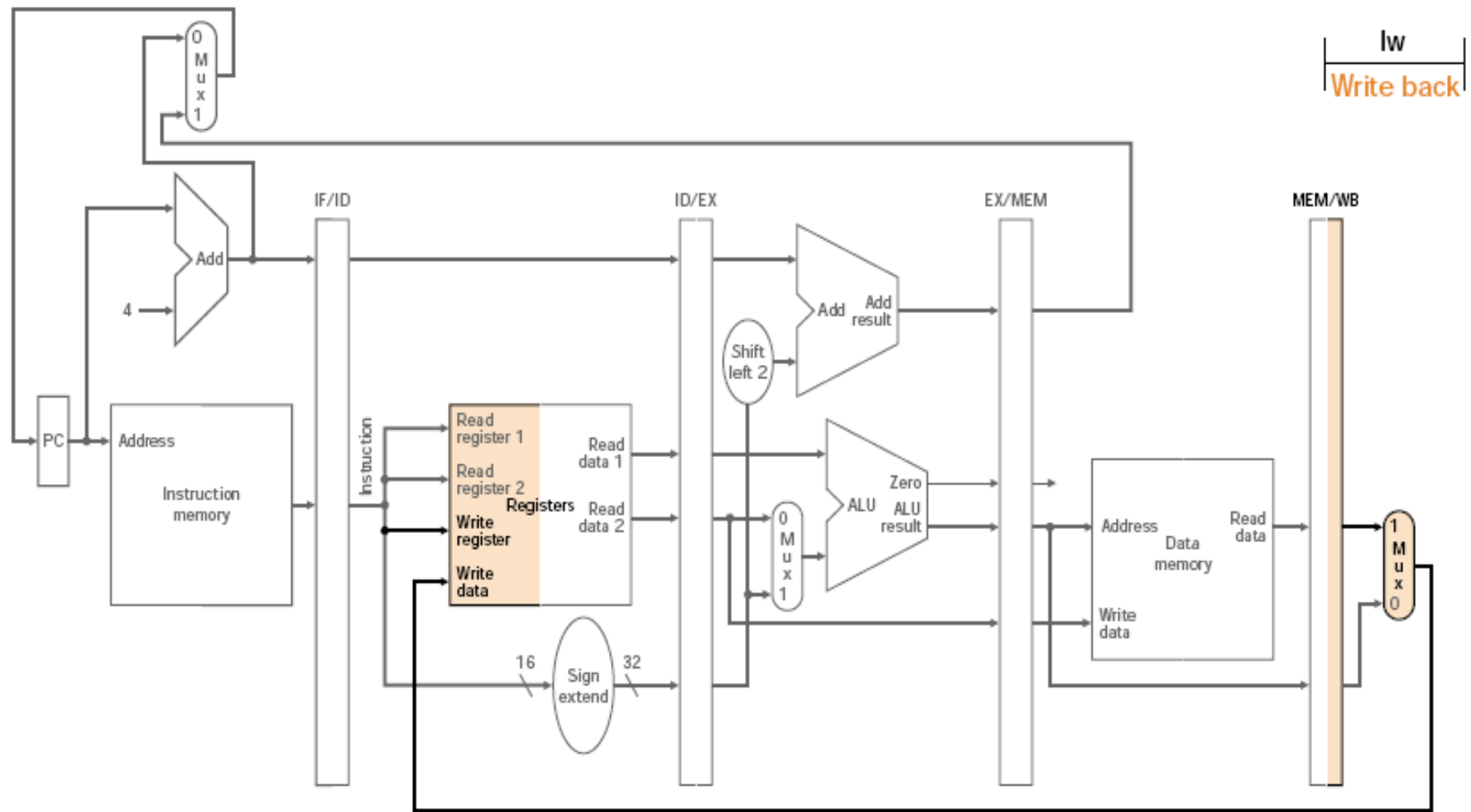

Problem?

Iw Writeback: bug fixed

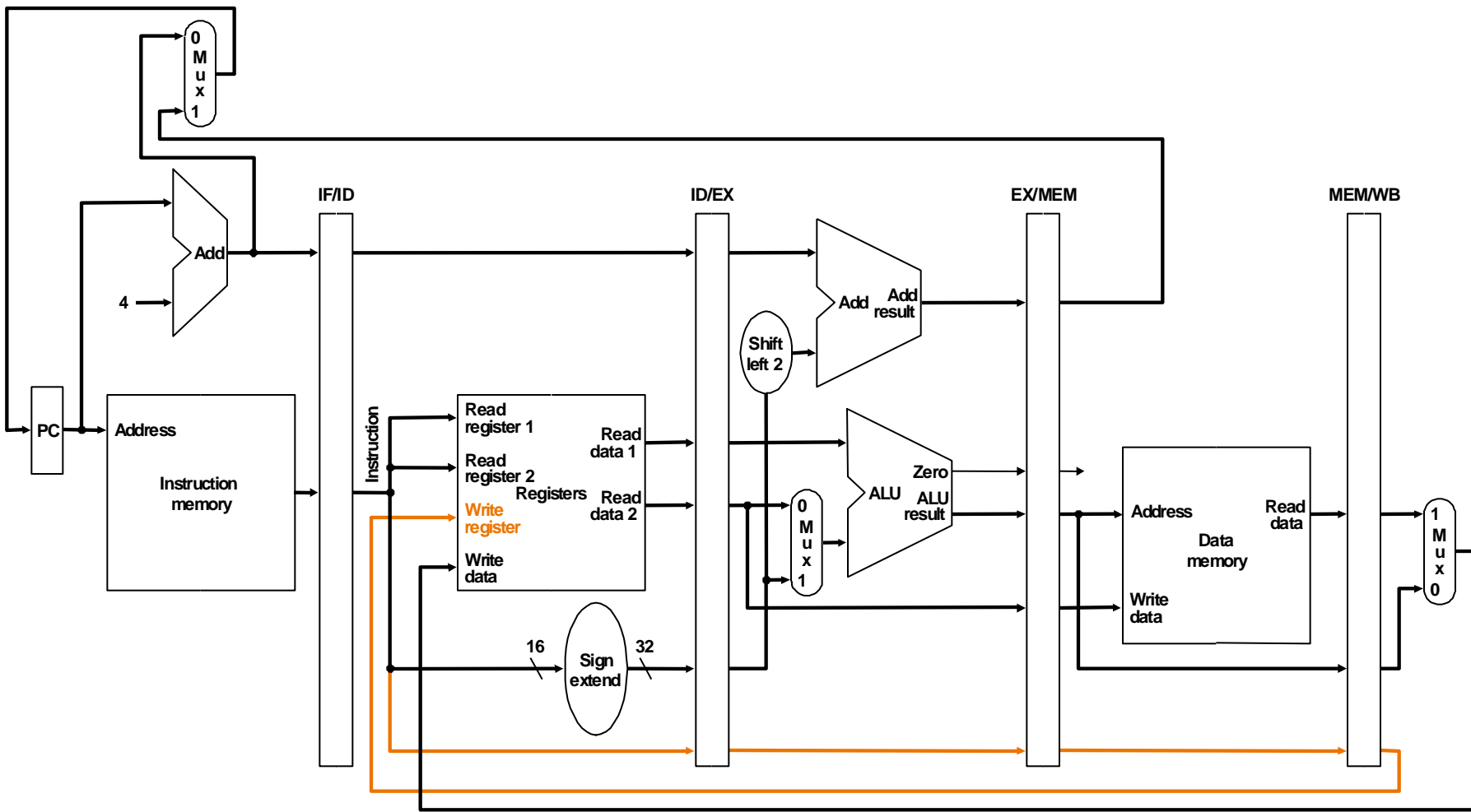

Pipelined Datapath w/Control Signals

